

Next-Generation Energy Harvesting Electronics: Holistic Approach

Workshop and Showcase


Imperial College London, 11th February 2013


Efficient and adaptive power electronics for Energy Harvesting


Plamen Proynov, Gyorgy Szarka

Steve Burrow, Neville McNeill



bernard.stark@bristol.ac.uk

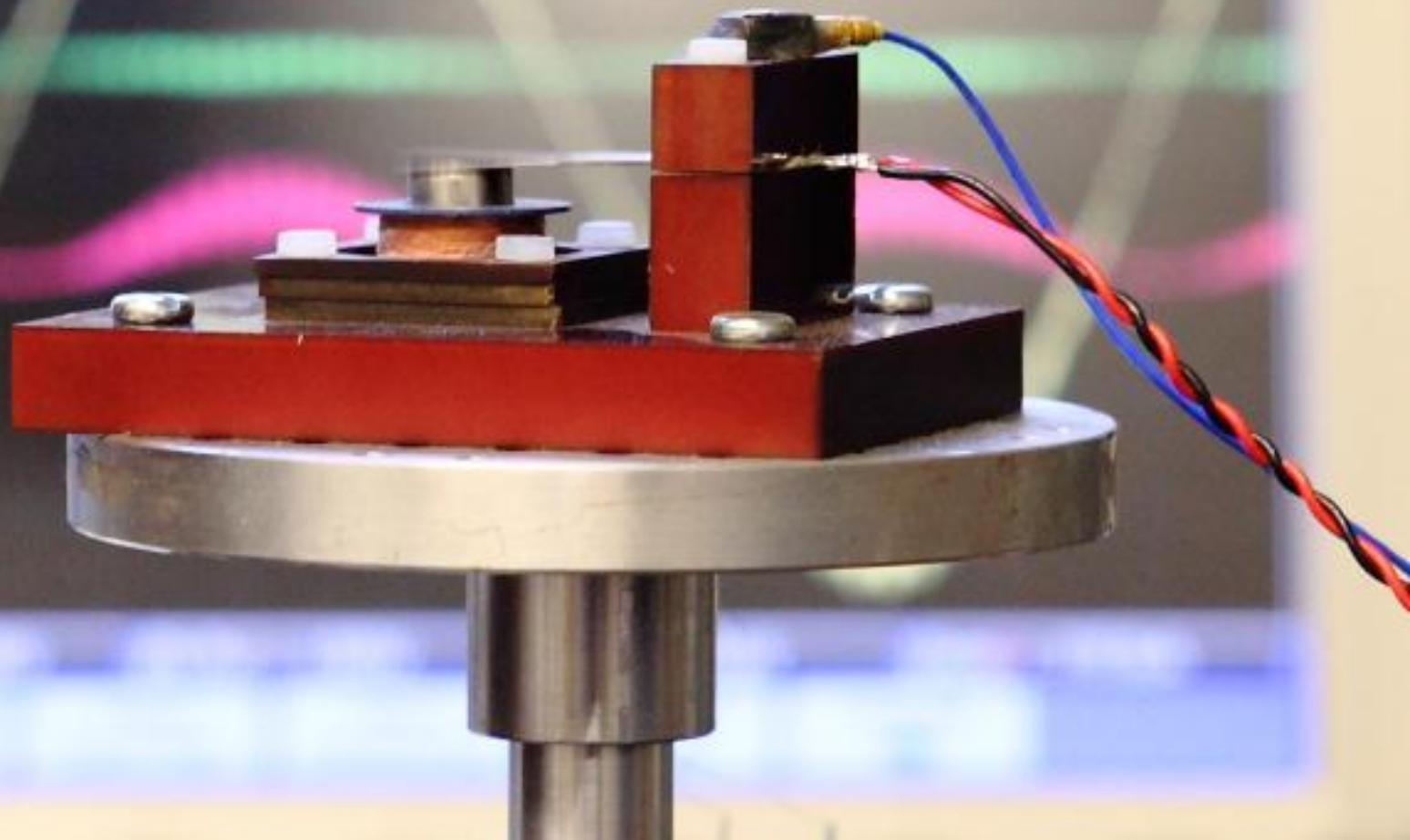

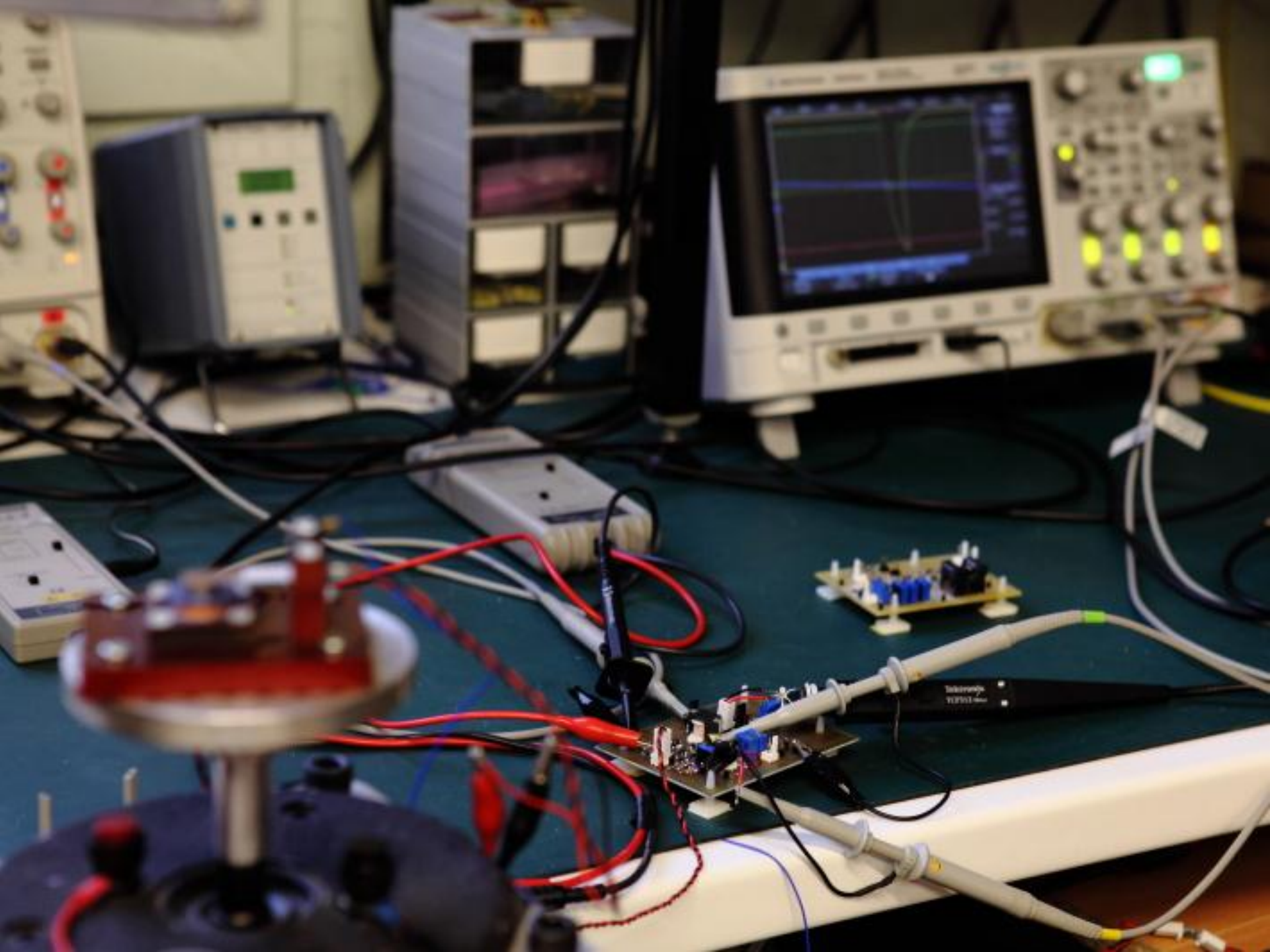


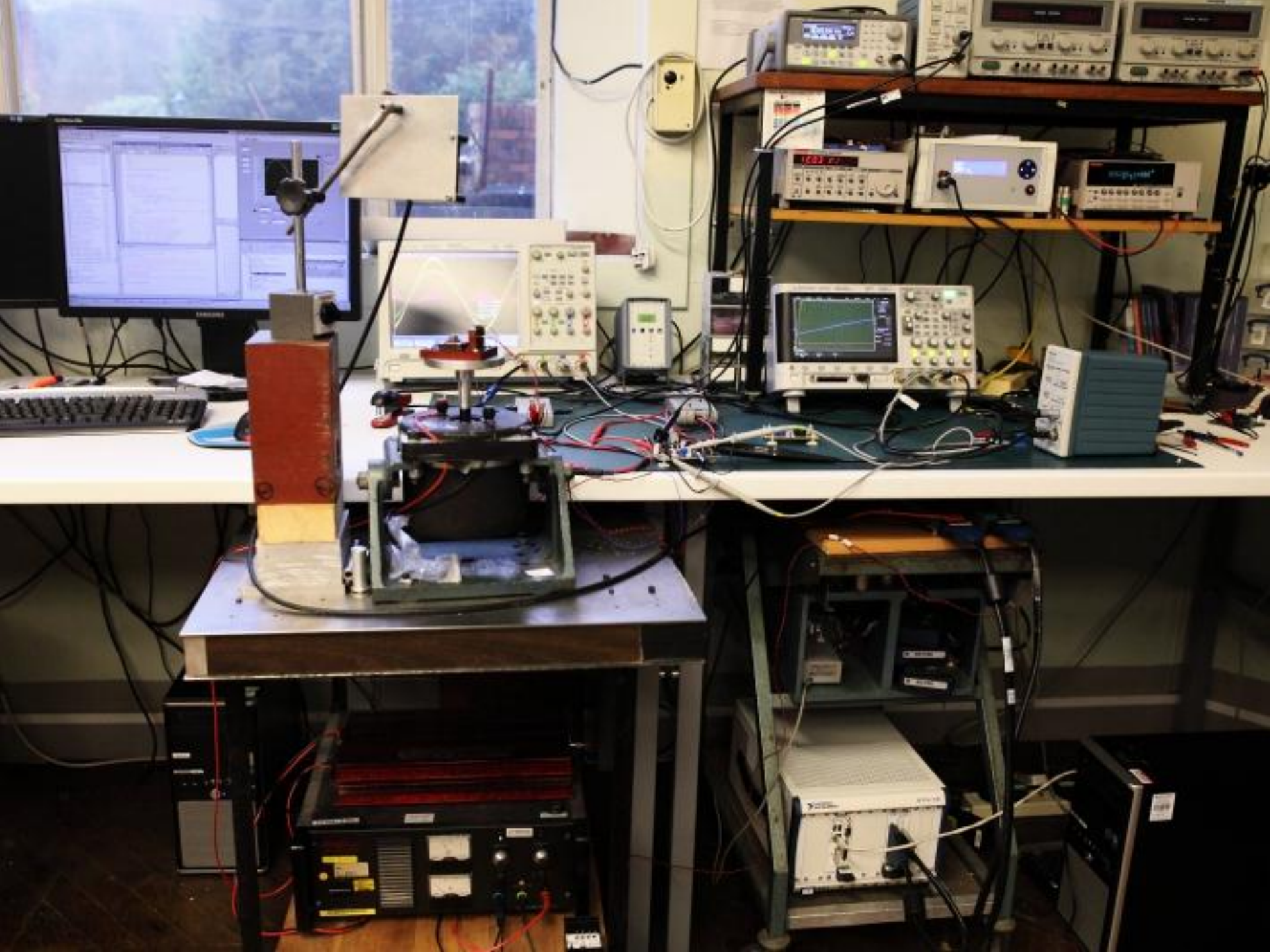


System operation from cold start

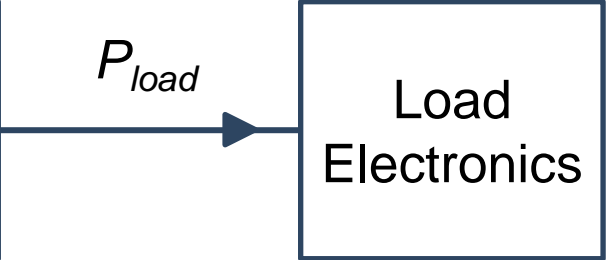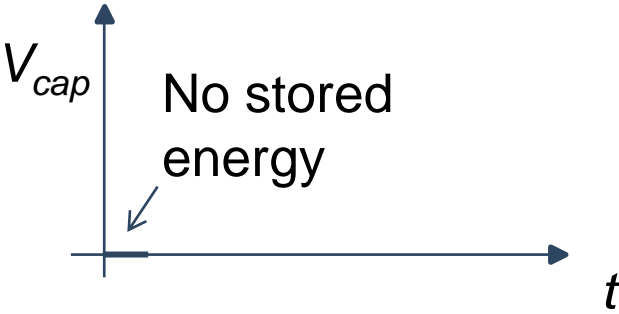


System operation from cold start

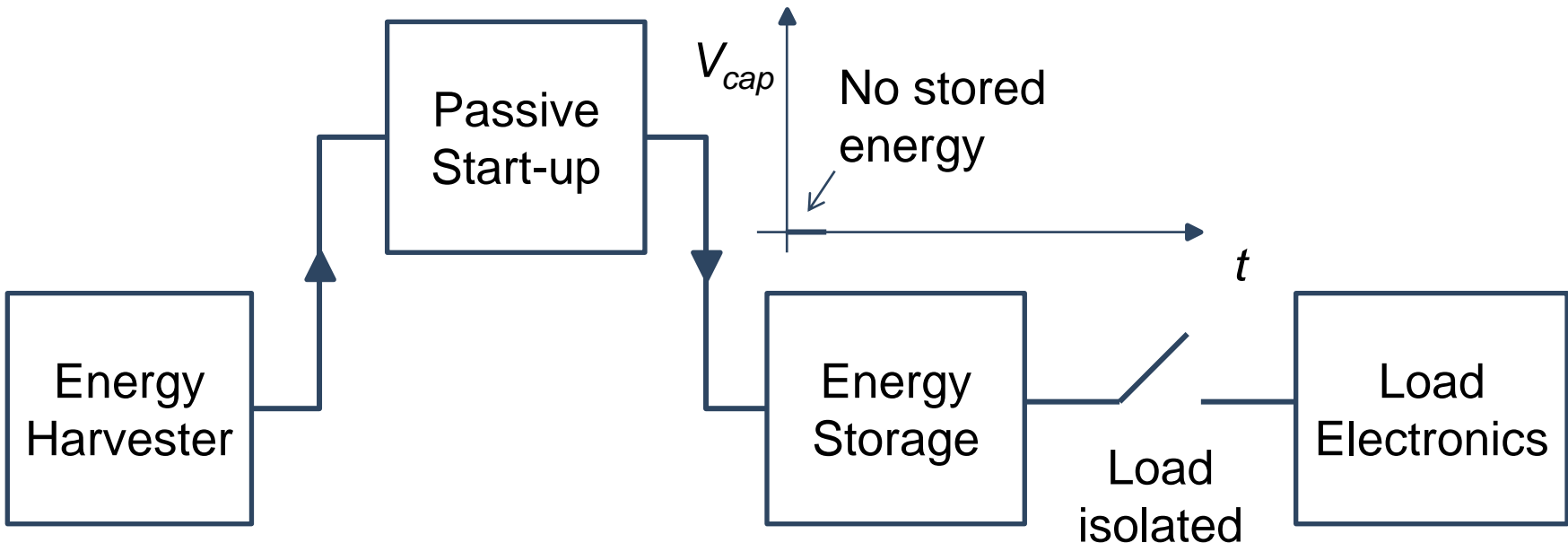


System operation from cold start

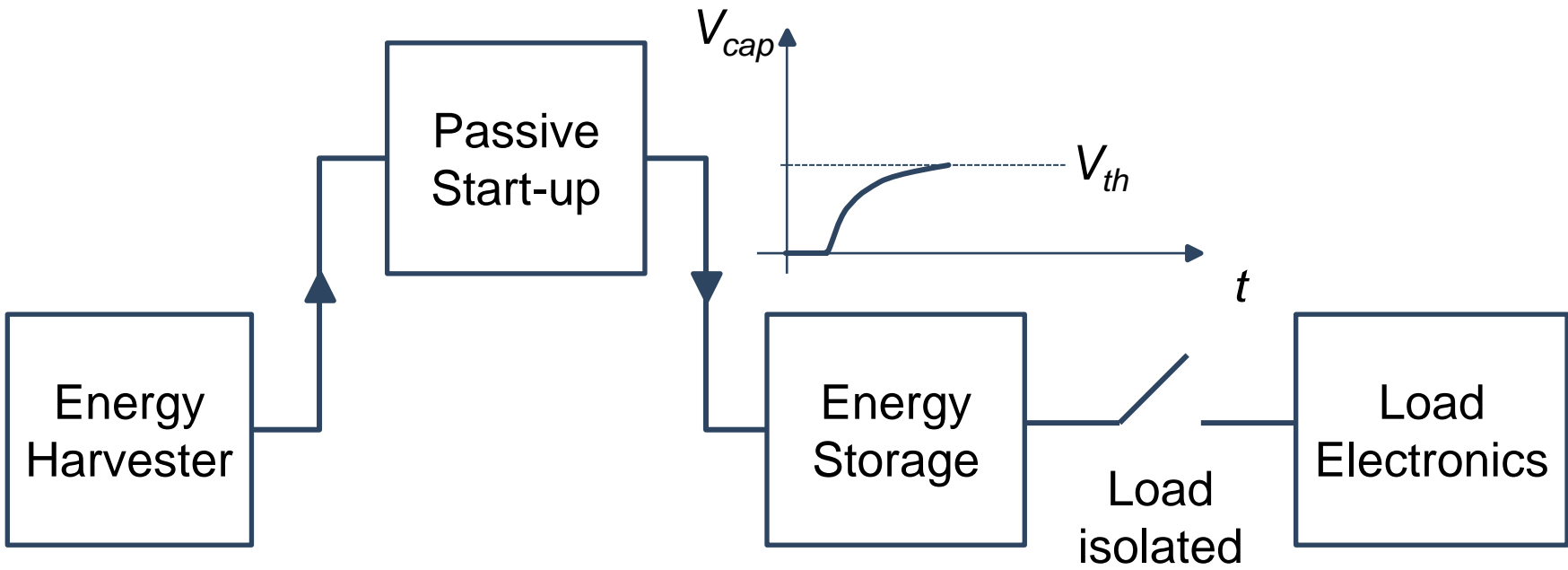


System operation from cold start

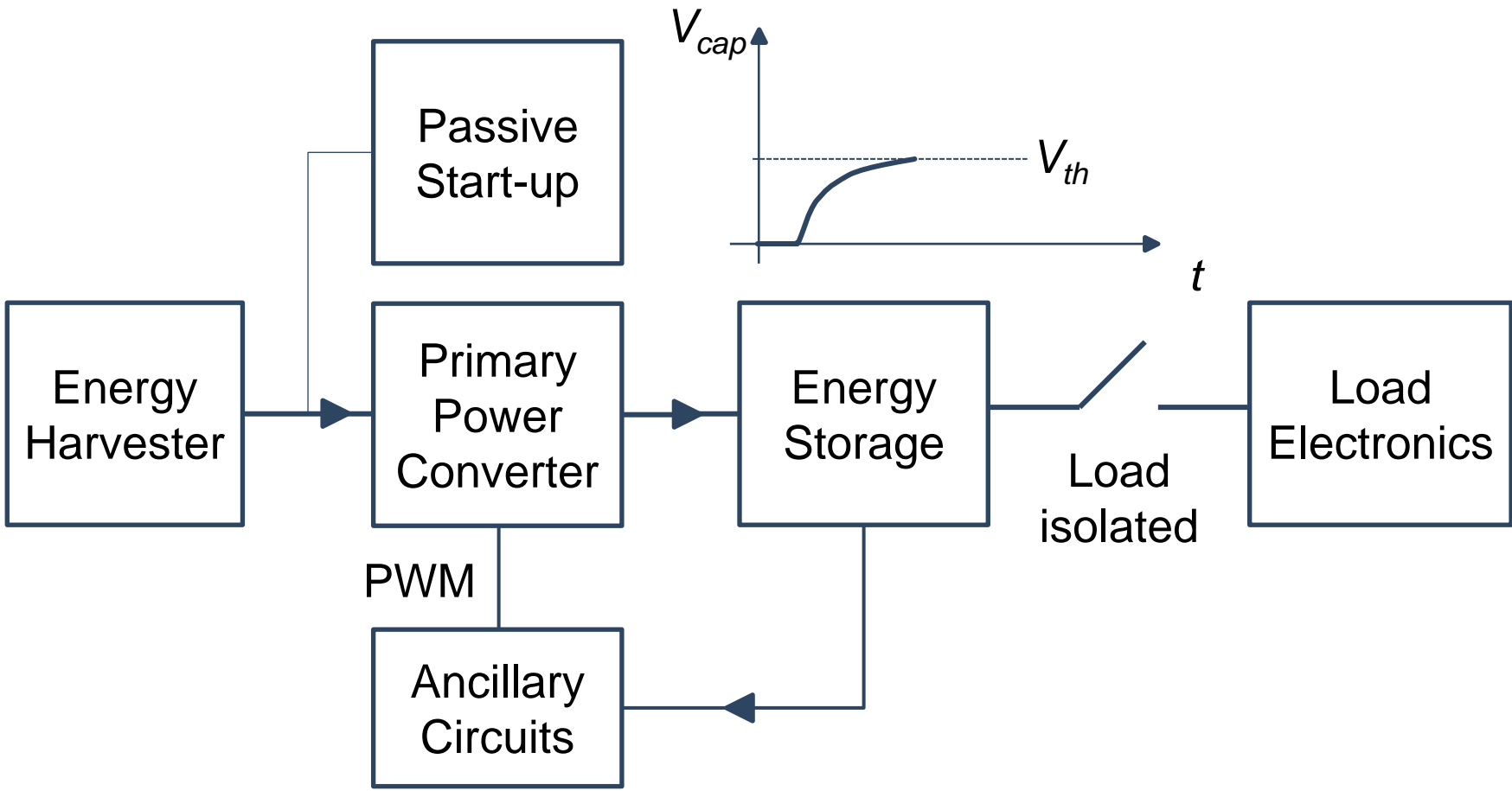


System operation from cold start

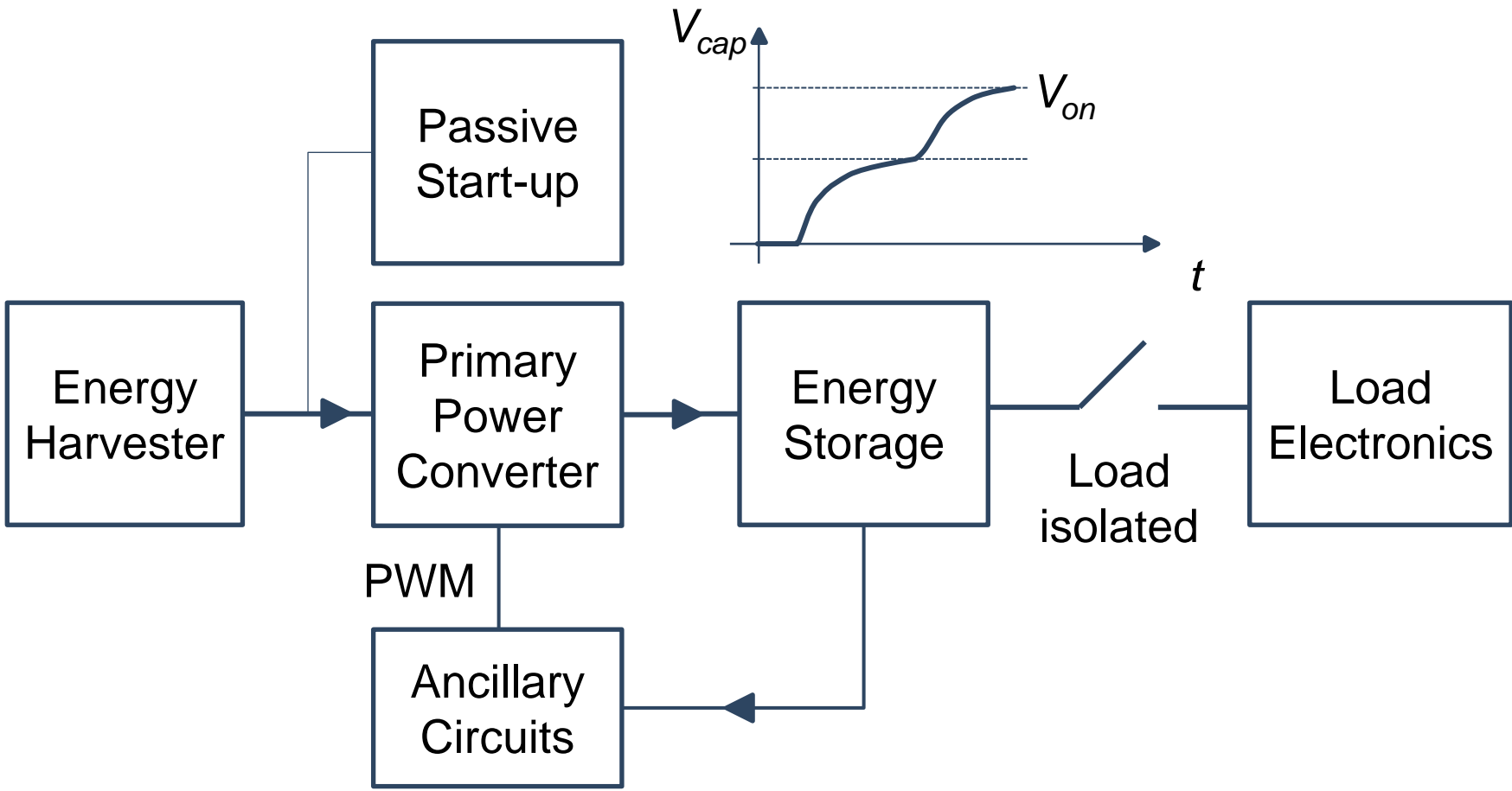

System operation from cold start

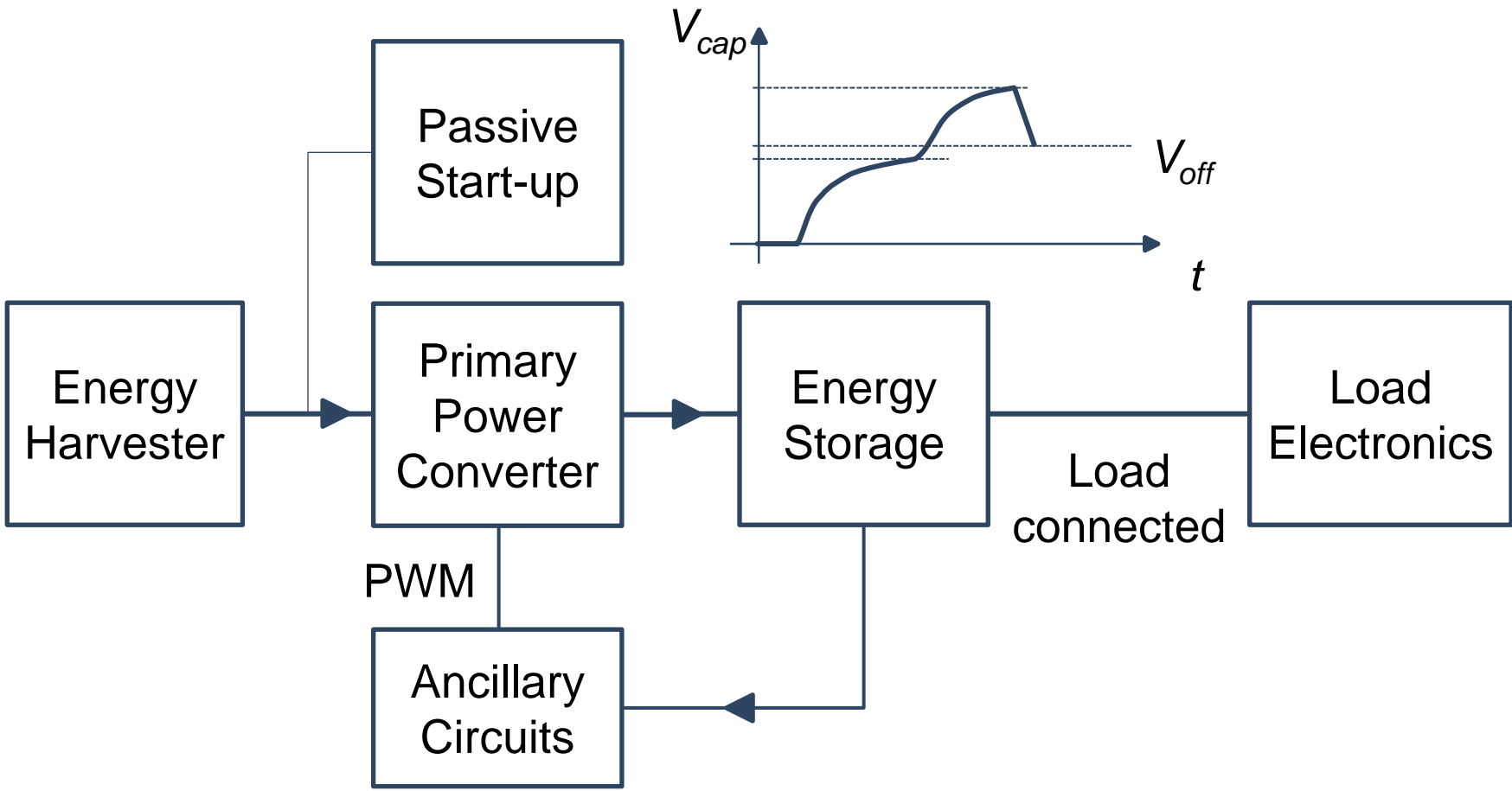


System operation from cold start

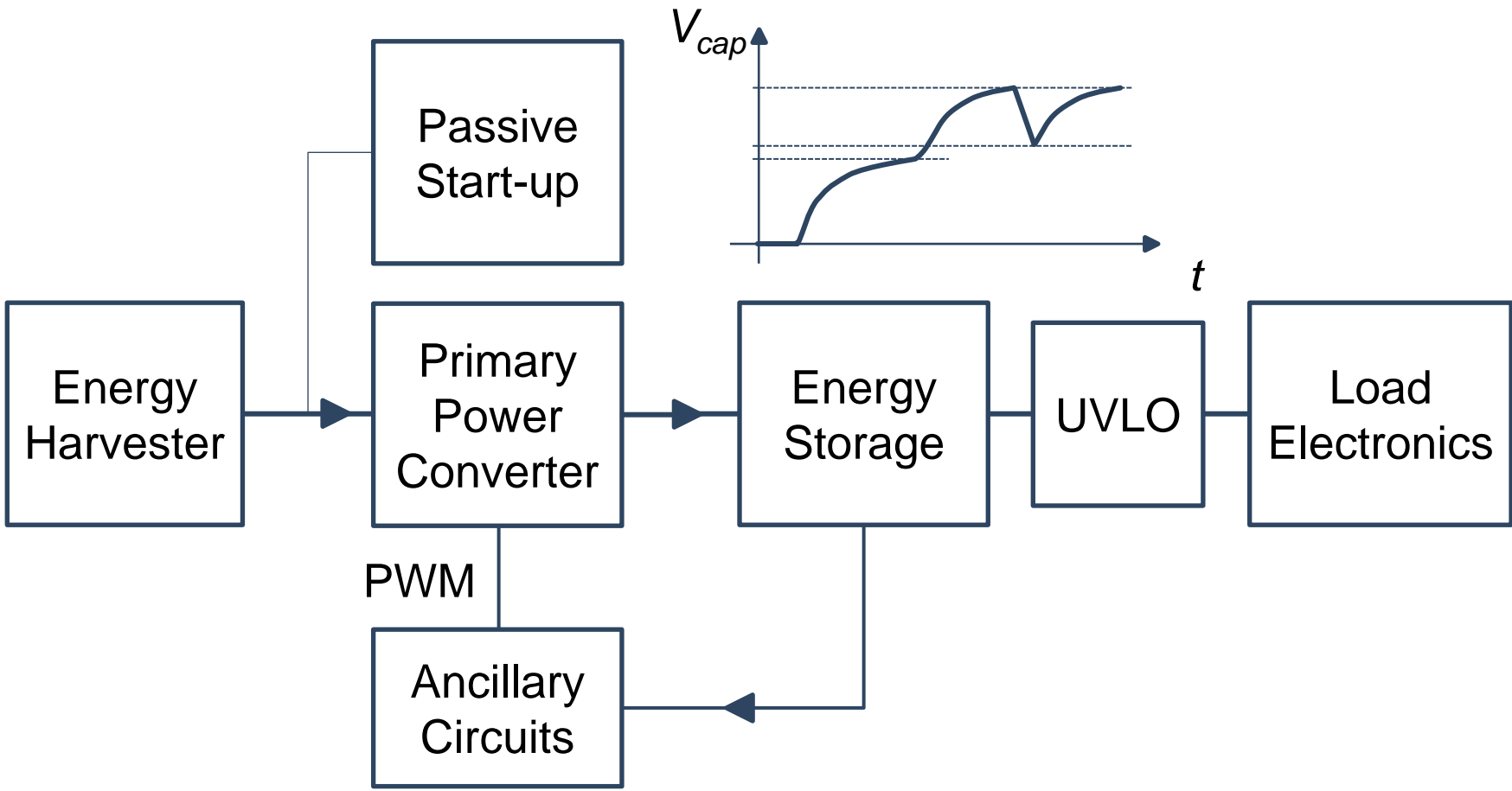


3 cycles and their time scales


Voltage boosting
×10

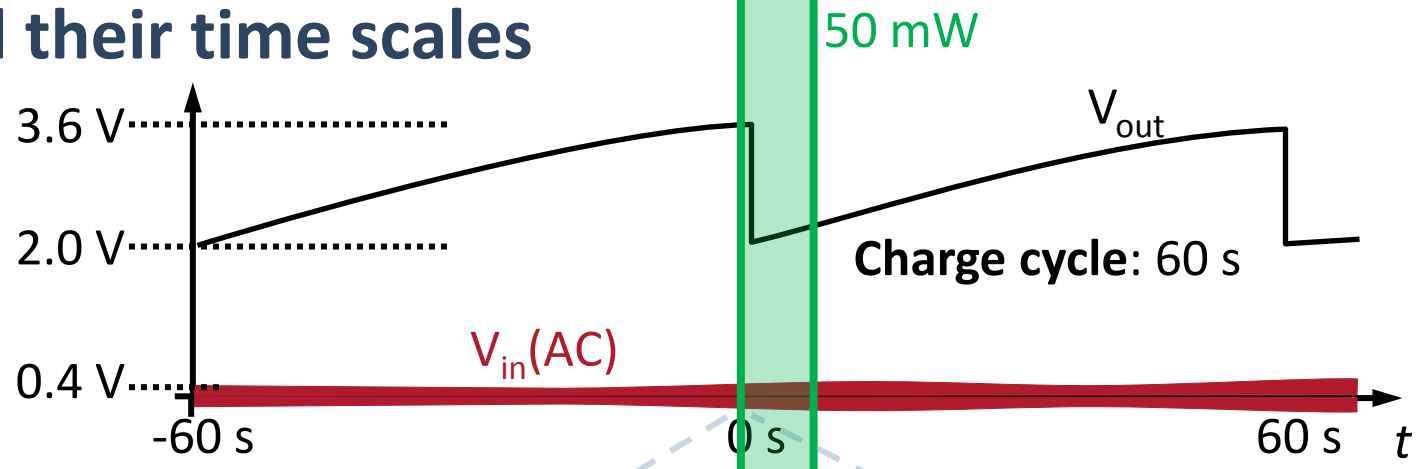


Power boosting
×1000

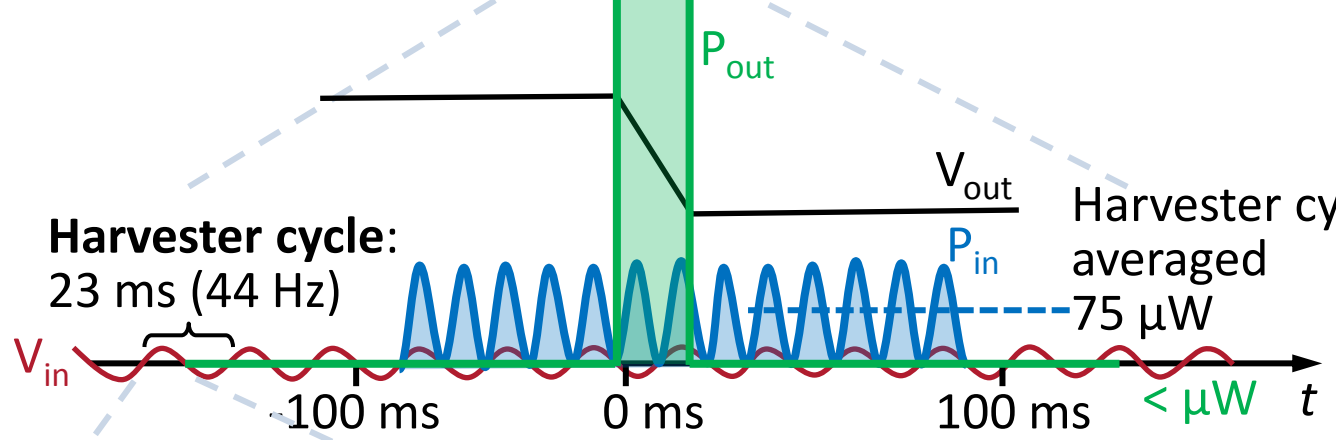


Switched-mode conversion

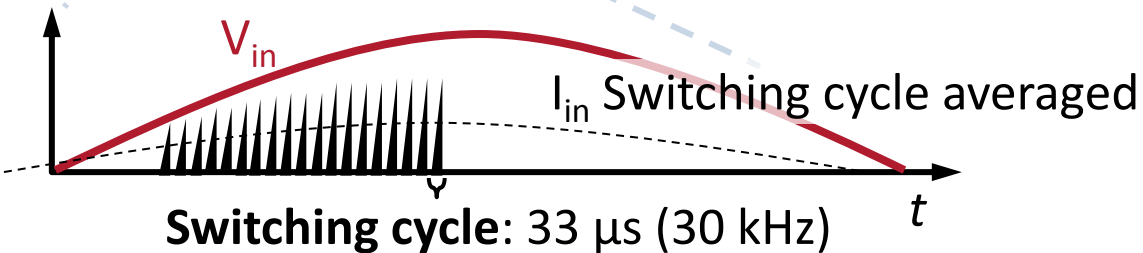


Low-power implementation

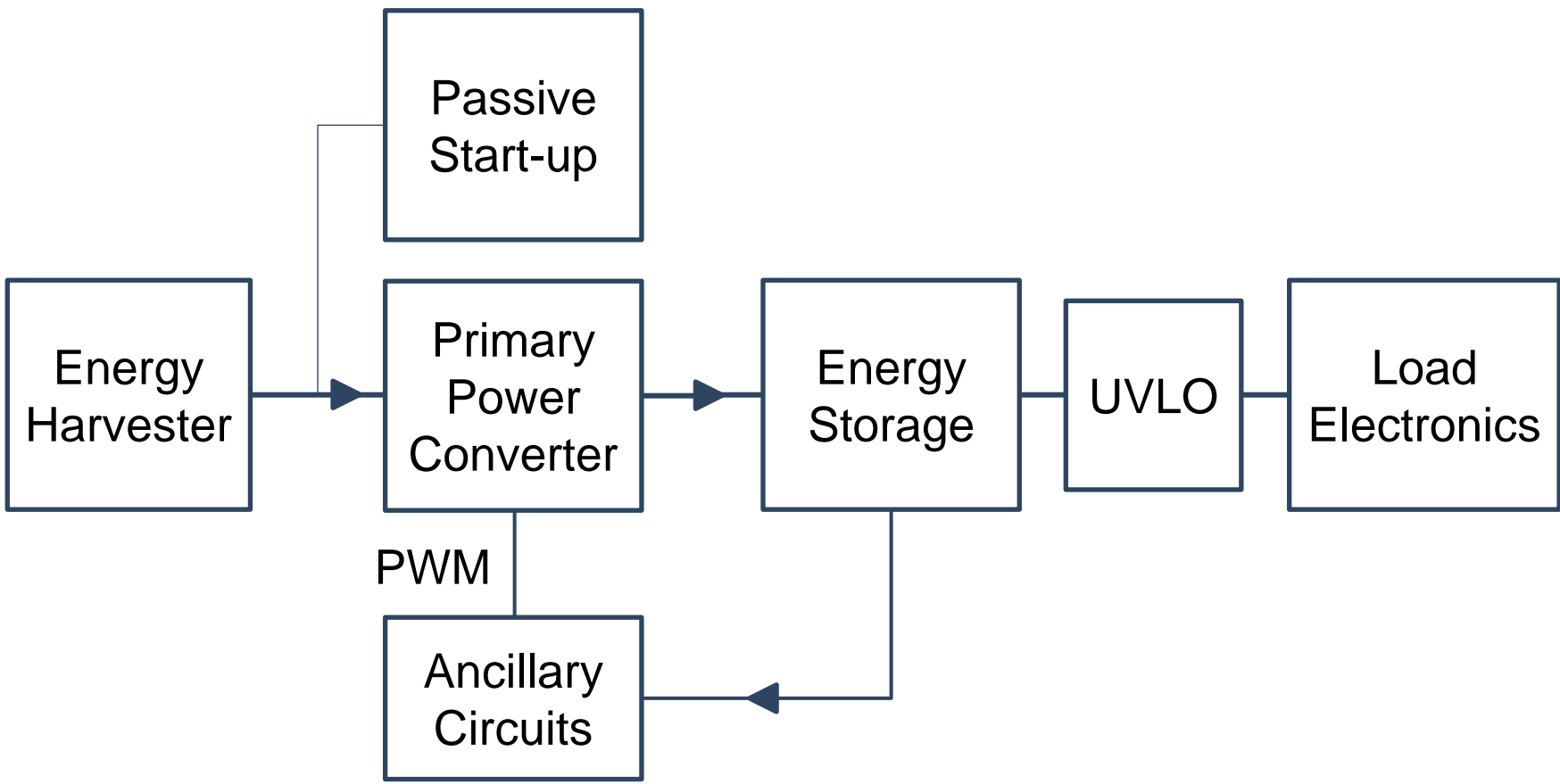


Low-power implementation

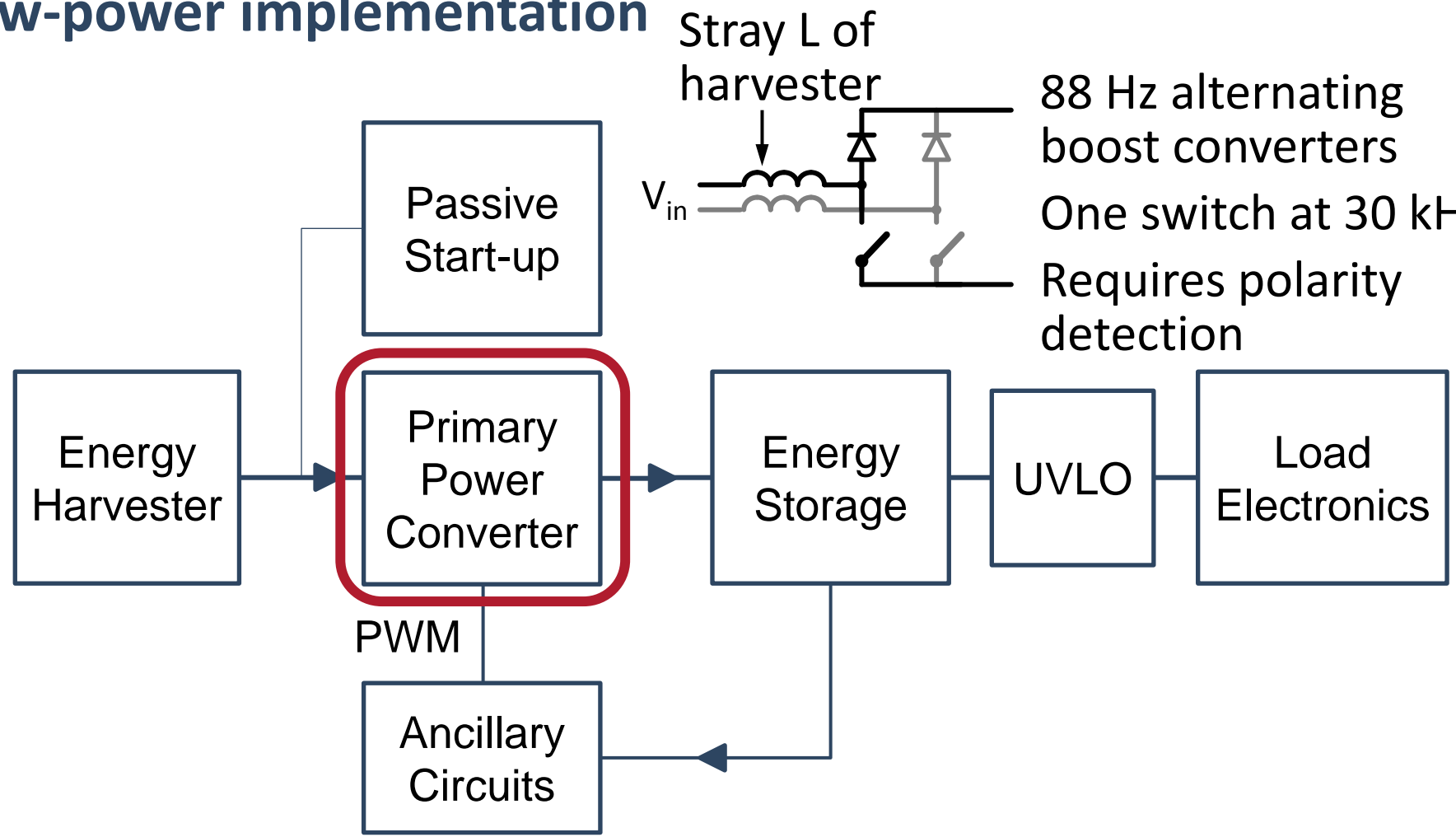

Low-power implementation

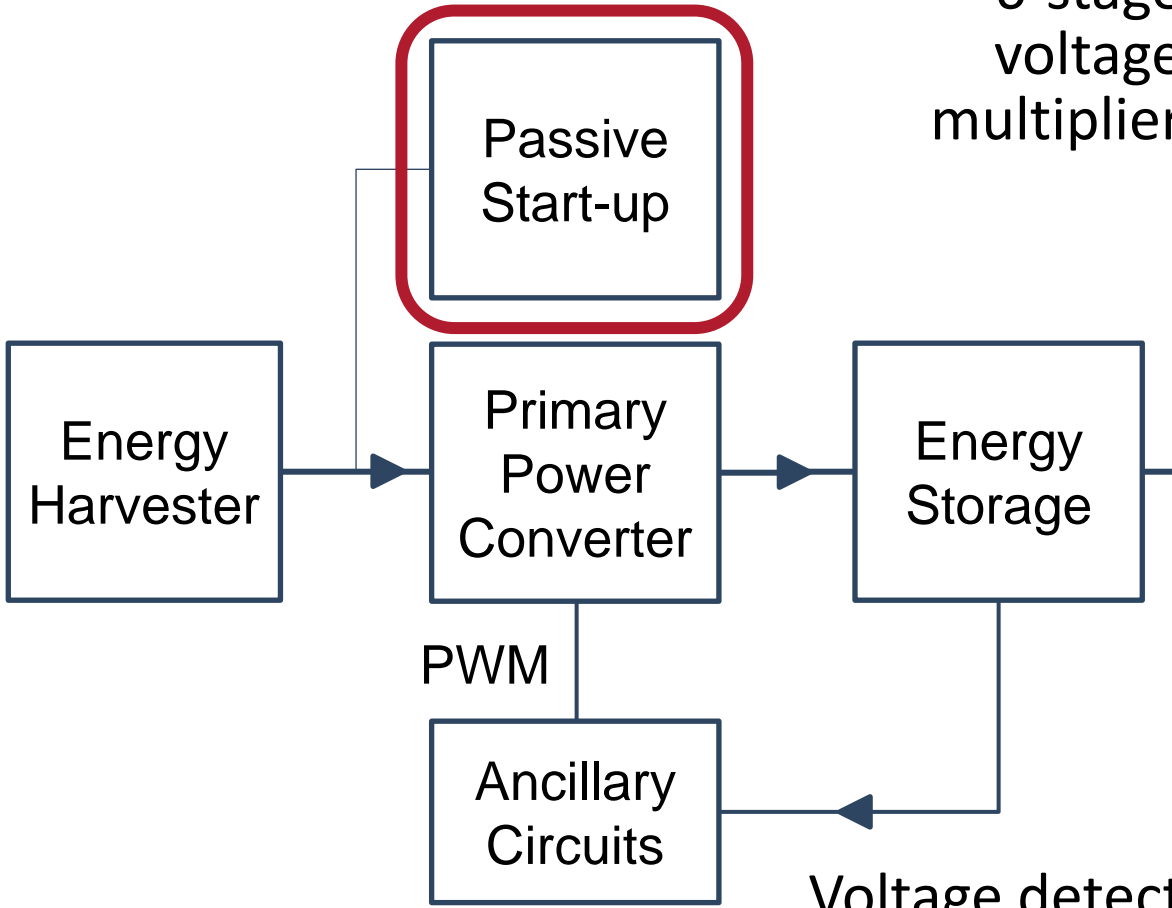


6-stage
voltage
multiplier


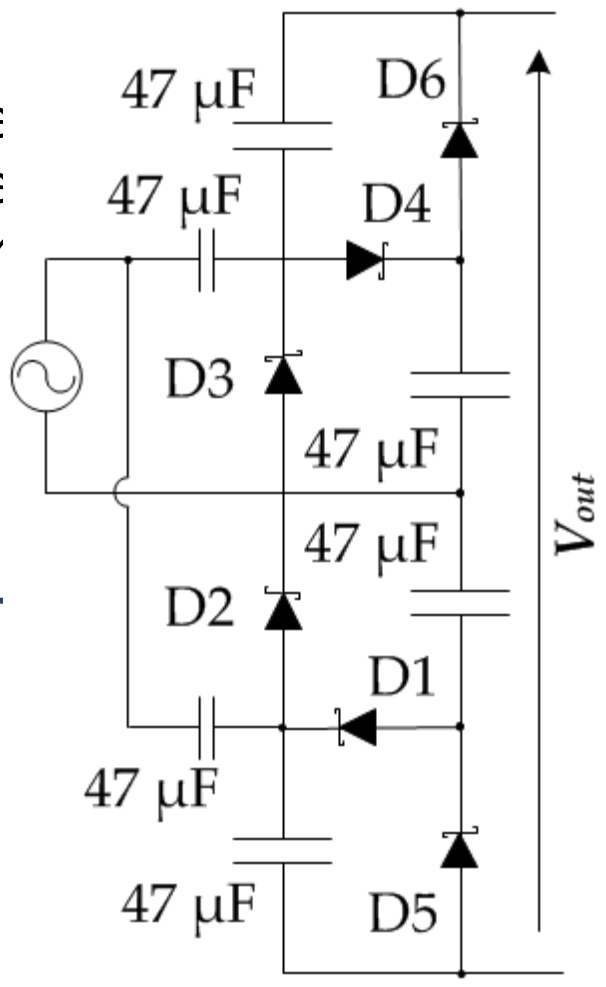


Voltage detector power-gates the μC
 μC controls activation of ancillary
circuits and isolates voltage multiplier
via JFET isolation switches

Low-power implementation

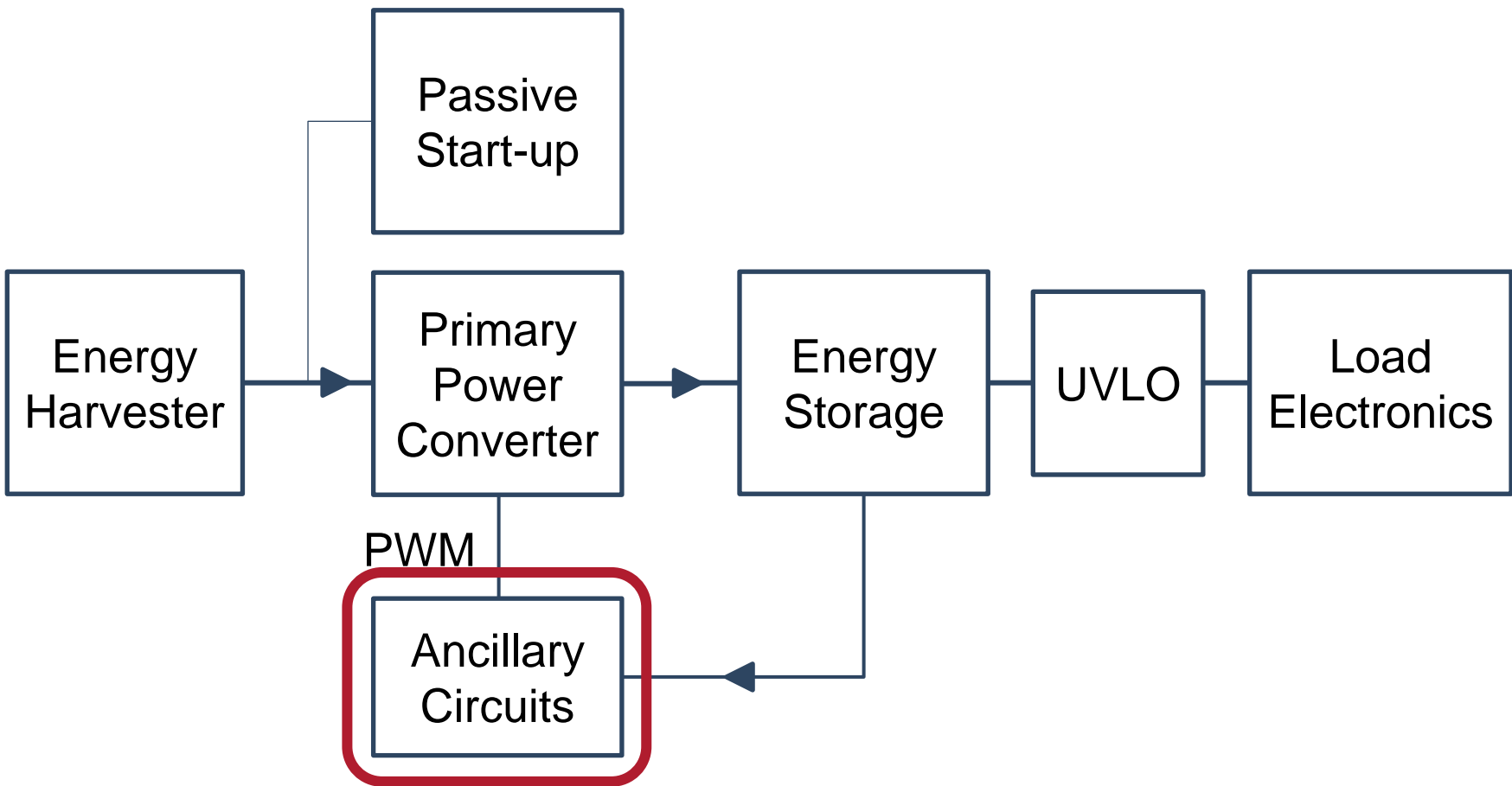

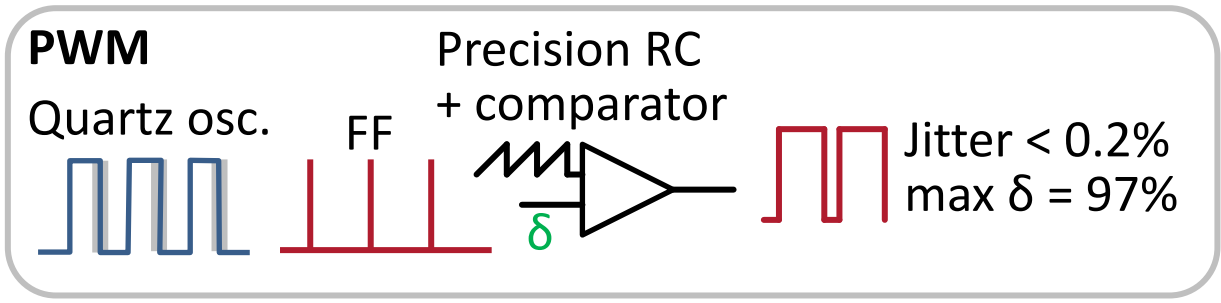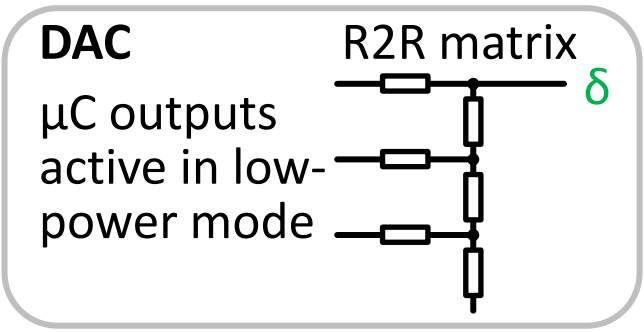Low power implementations: useful ancillary circuits





μC \curvearrowright LPM4 = 100 nA
max clock frequency


on once per 23 ms
harvester cycle for 4 μs

on once every 15 harvester
cycles for 34 μs to track
max power transfer:



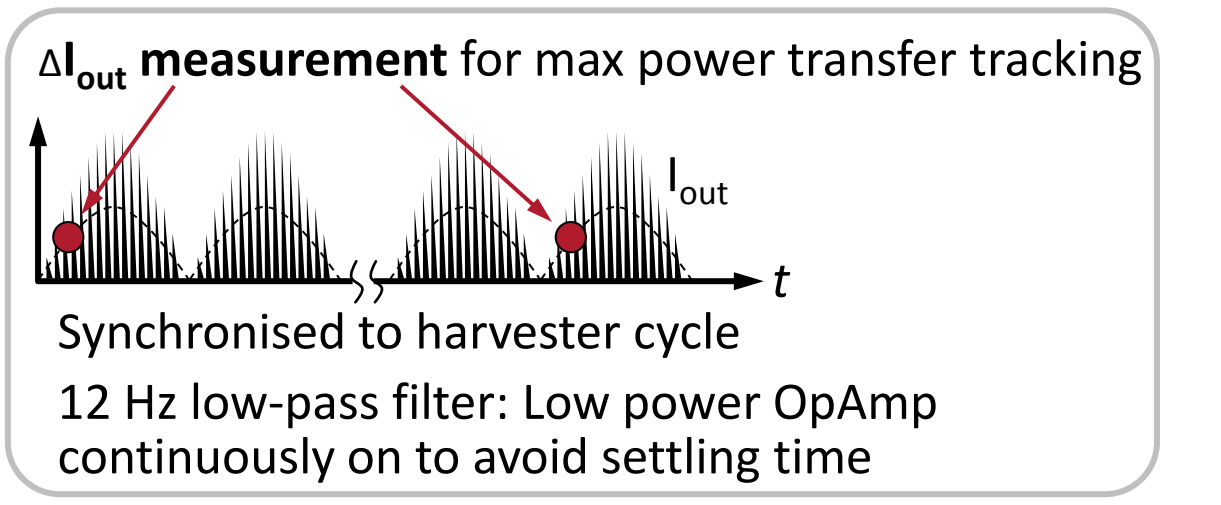
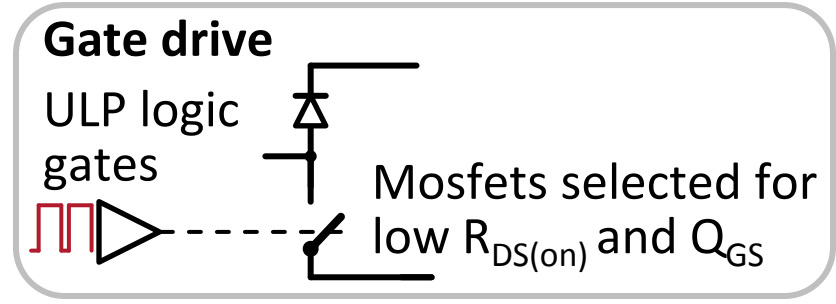
measure I_{out} , calculate
direction, perturb δ




Comparing control techniques

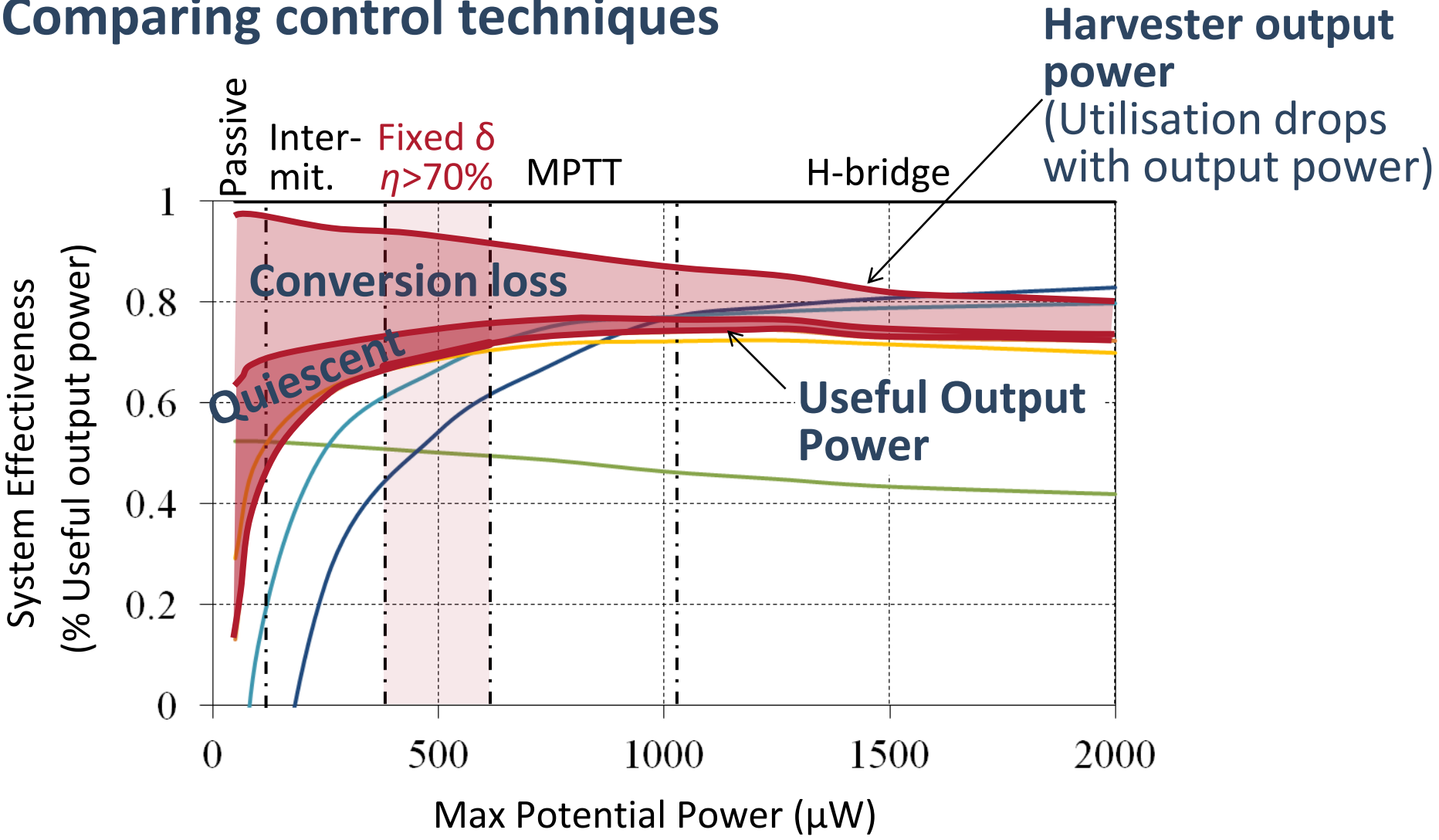



Options for adaptation

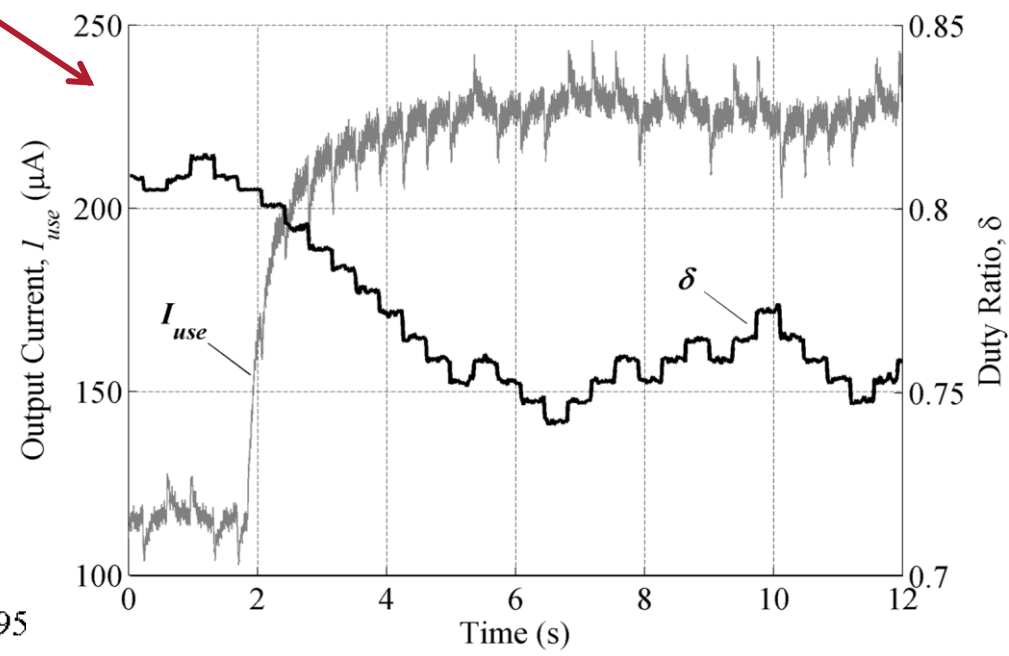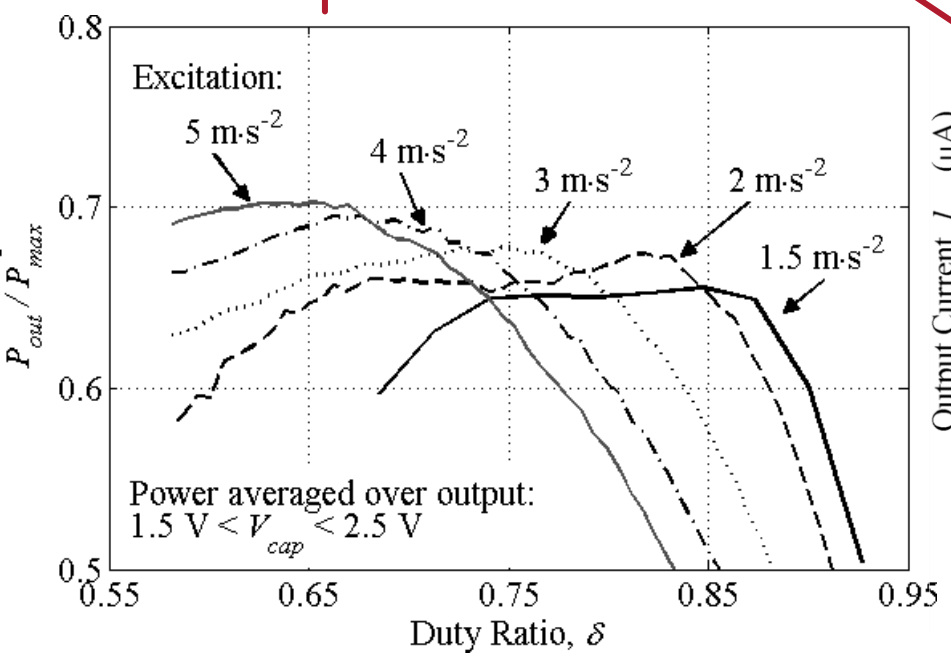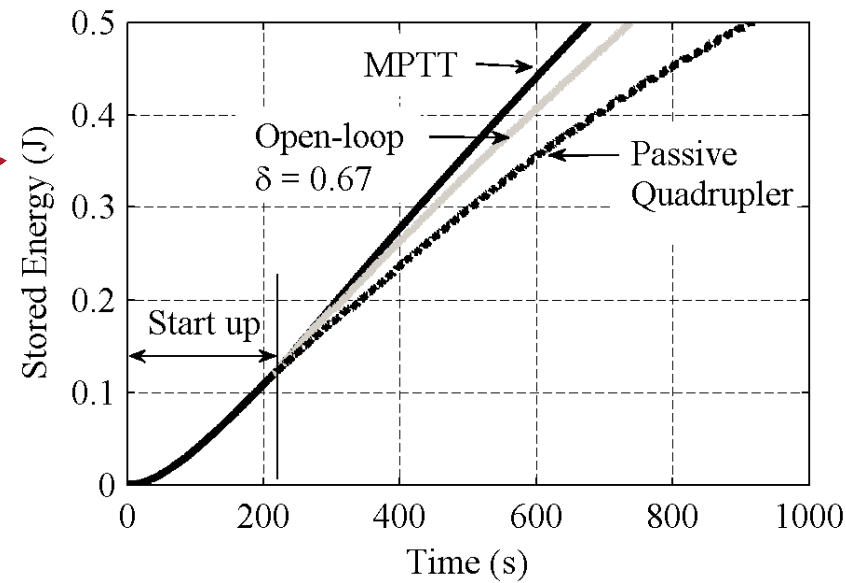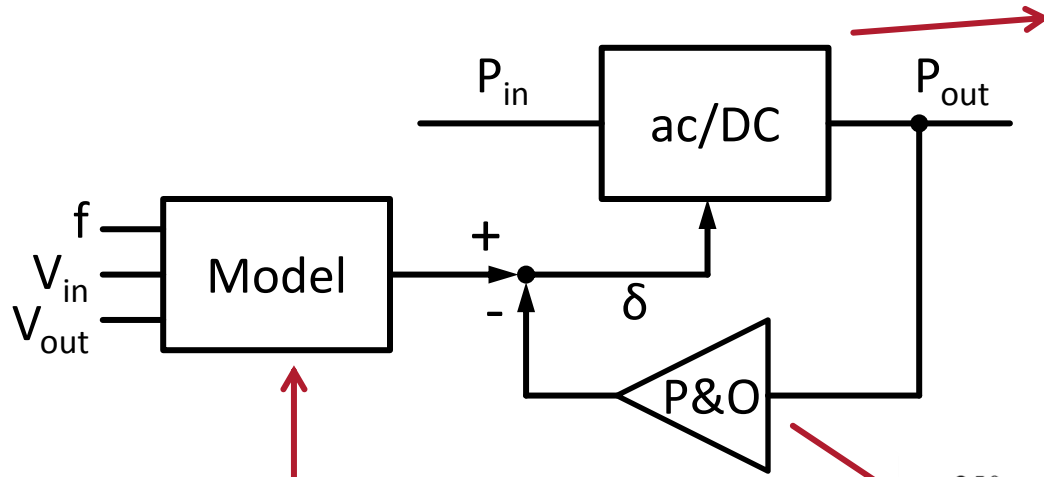


Slides for Q&A

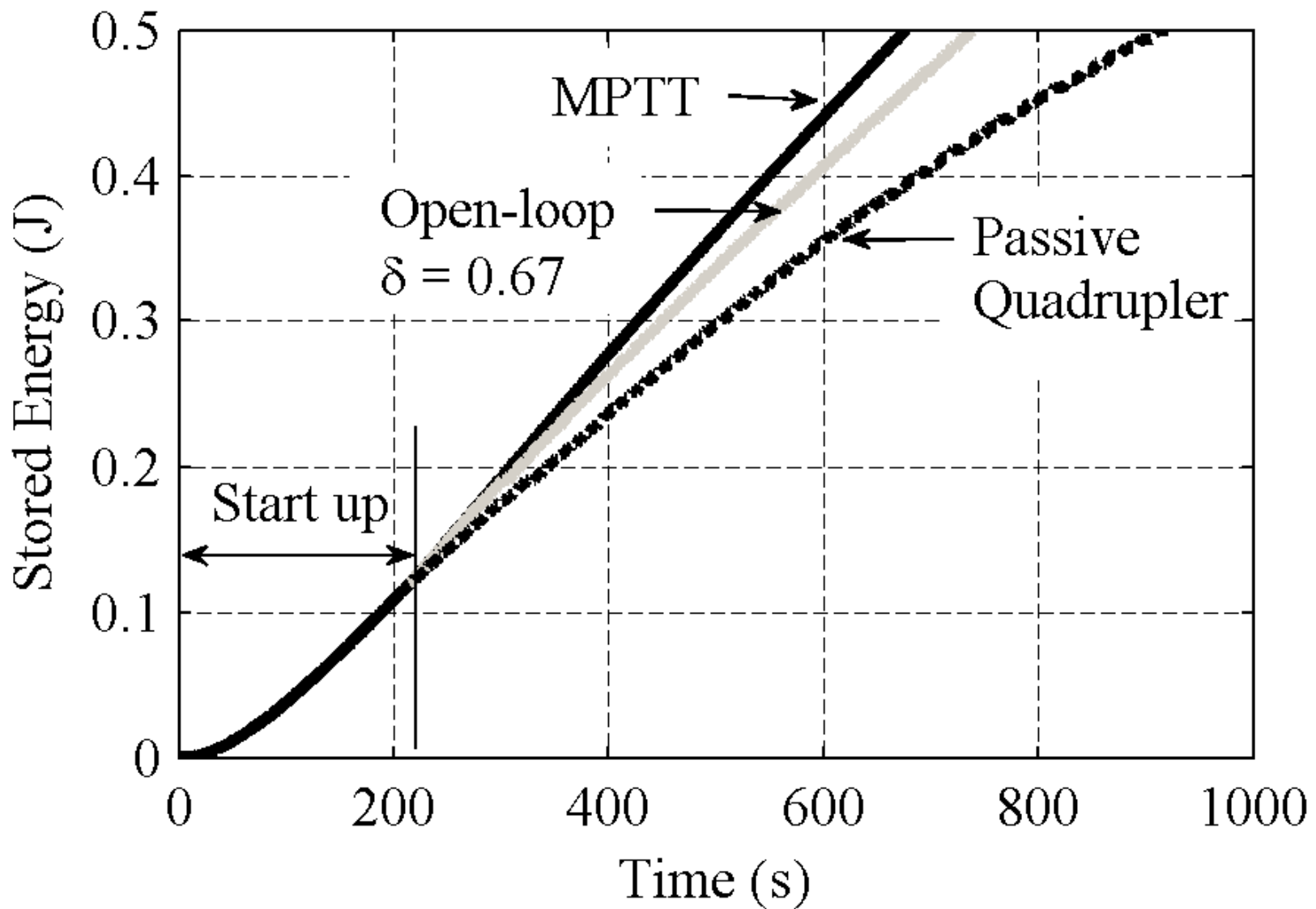


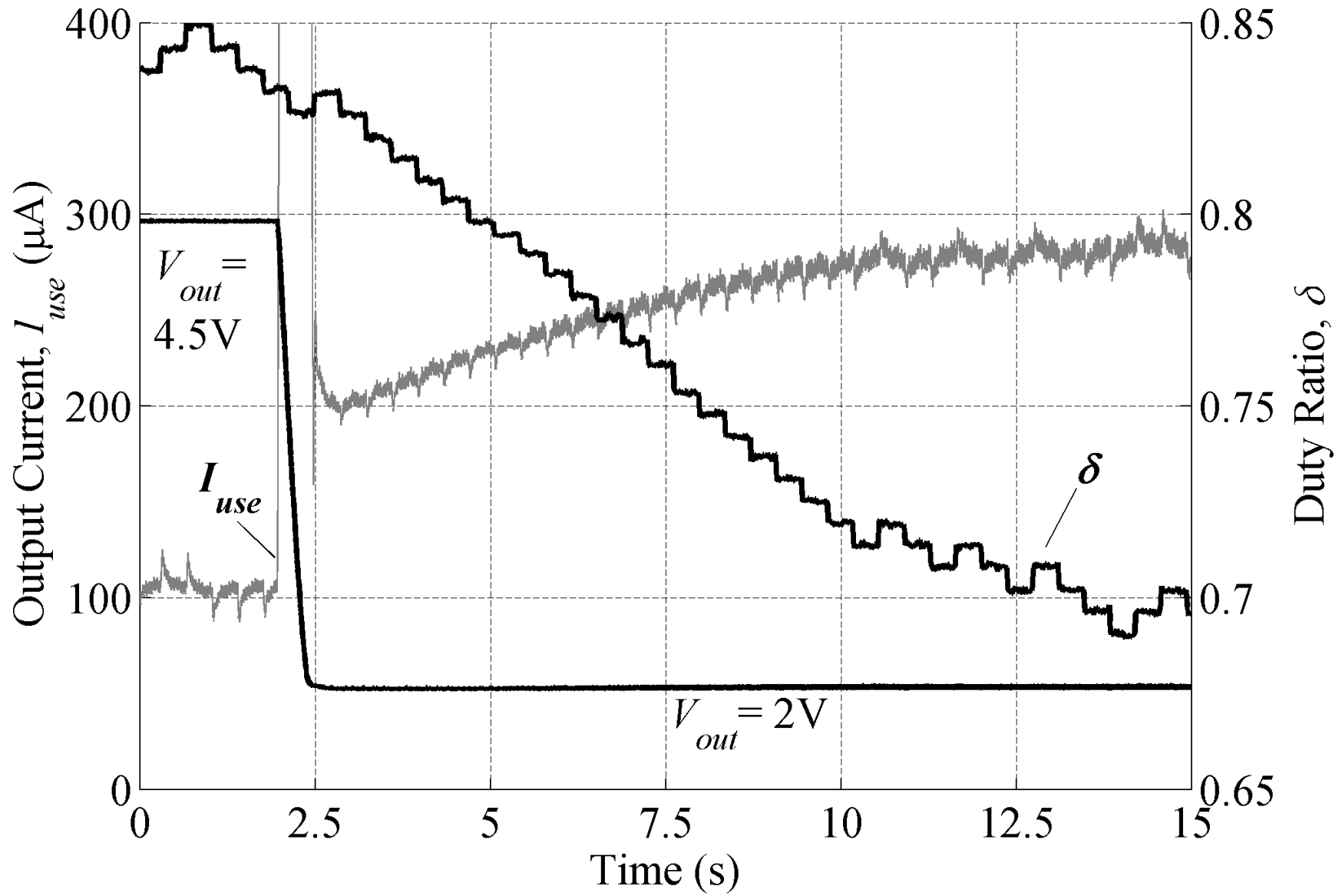

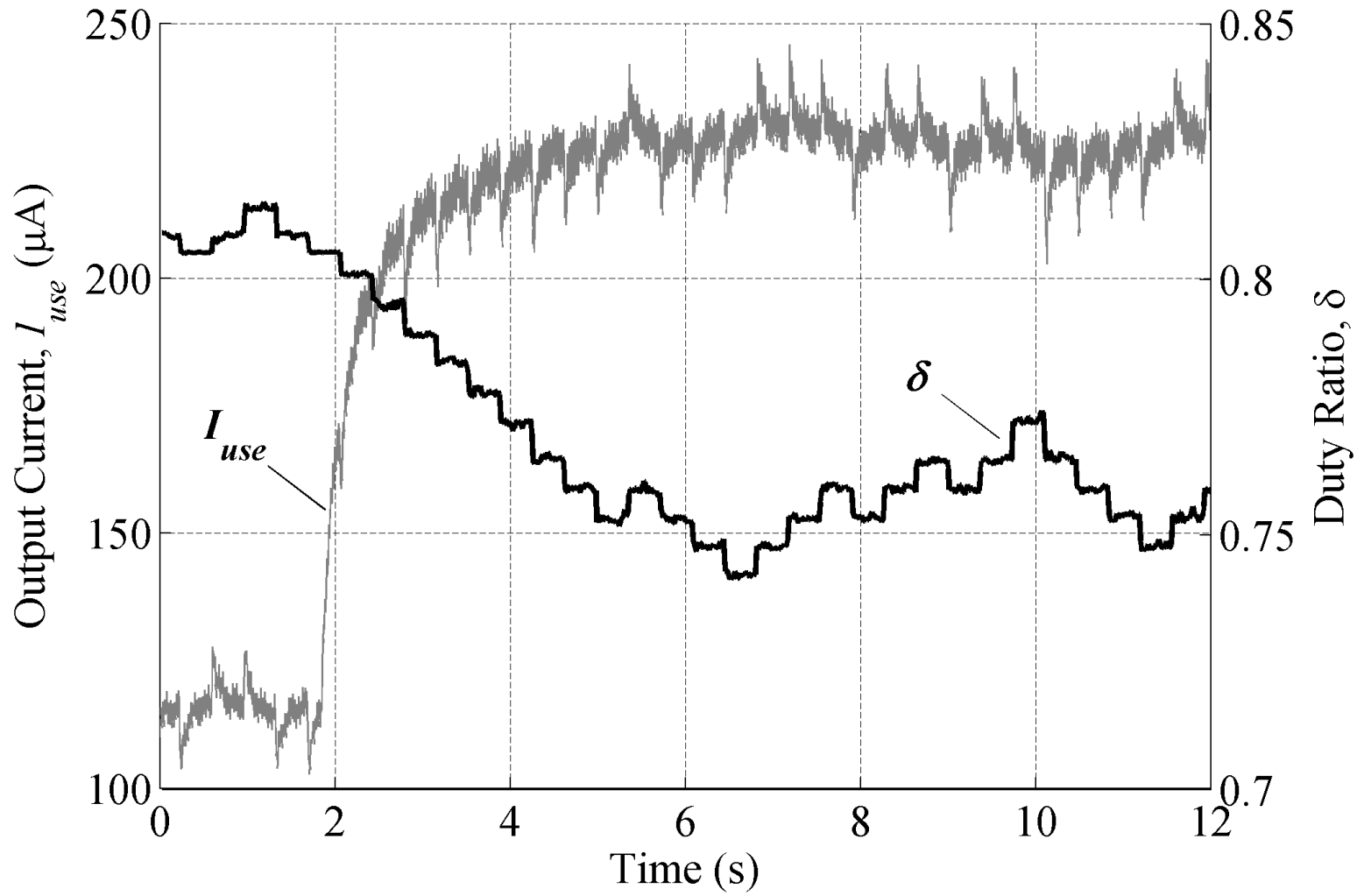


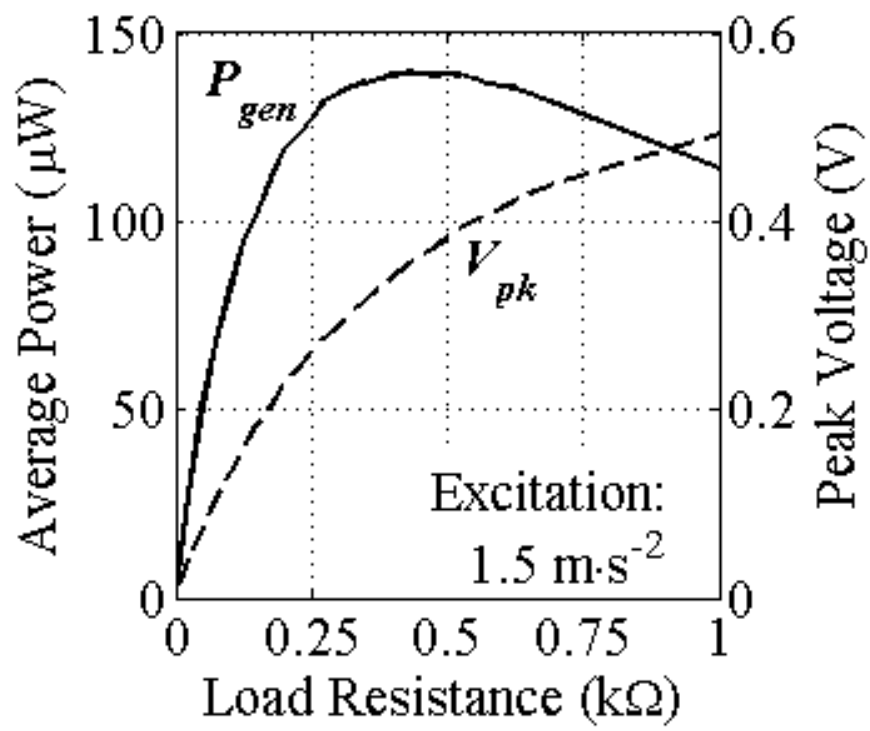


a)

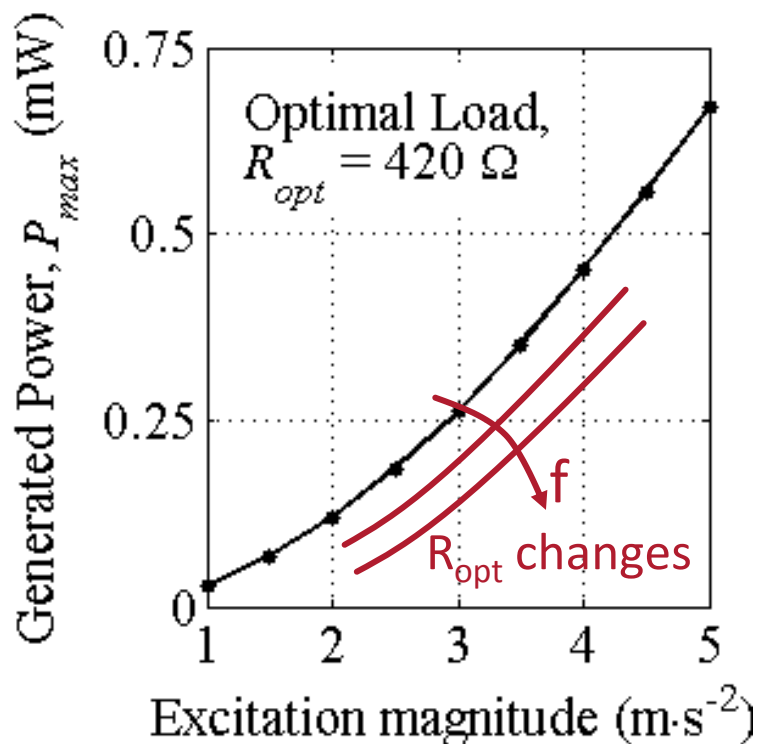

b)

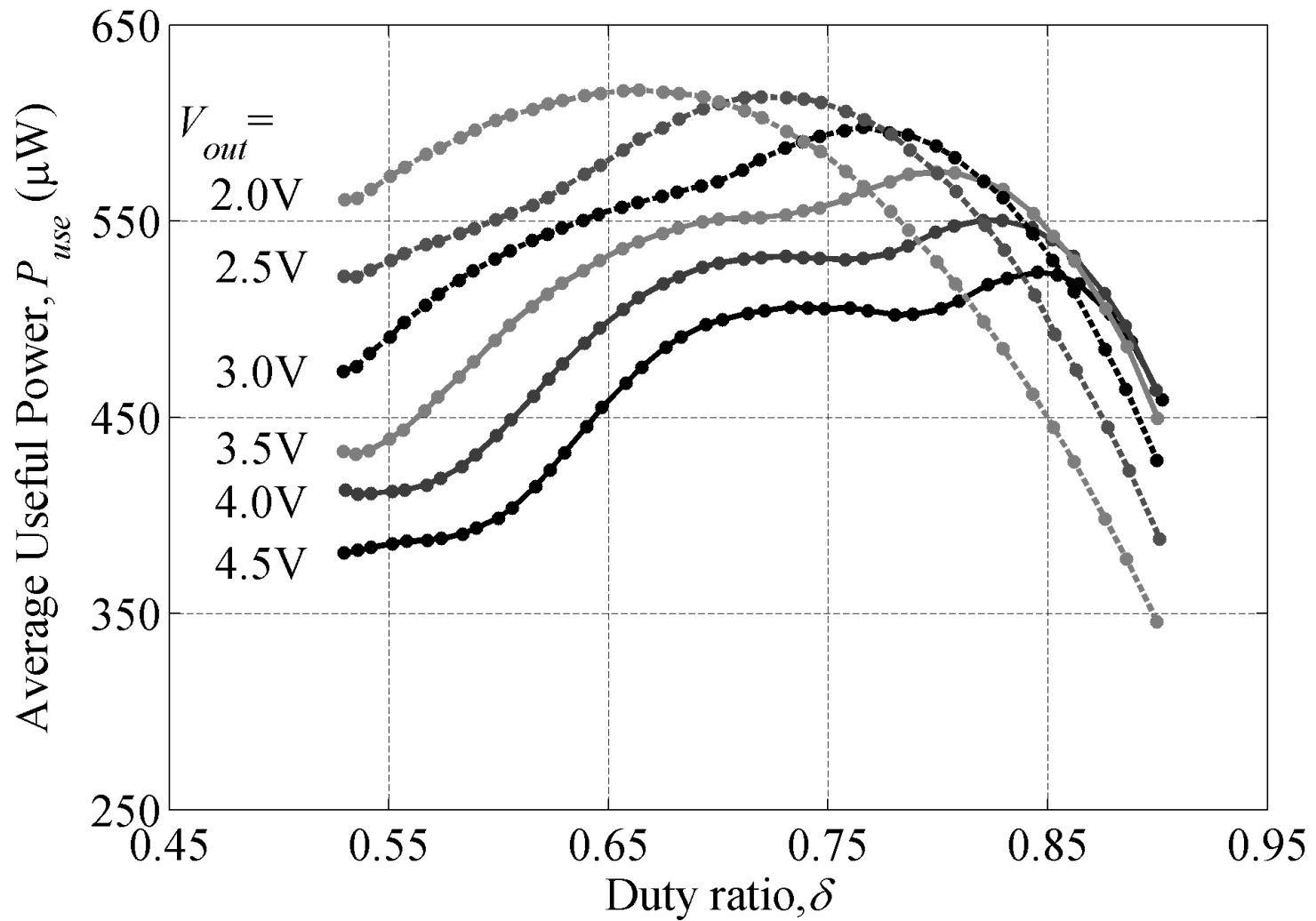

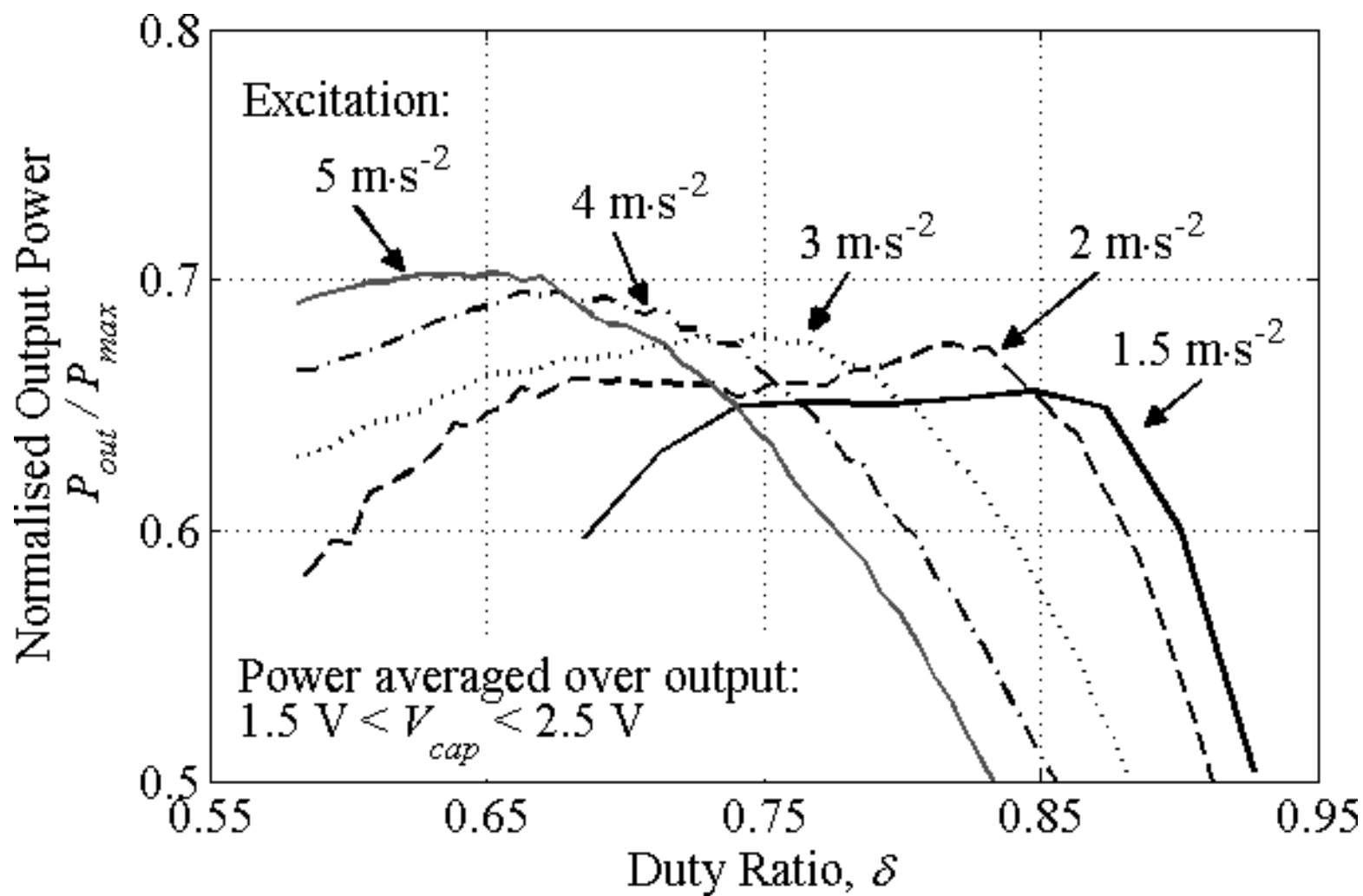


TASK A2 – INTERFACE CIRCUITRY FOR VIBRATION-DRIVEN ENERGY HARVESTERS

Main challenges

- Interface circuit design
- Matching circuit behaviour to harvester (impedances)
- Maximum power point tracking
- Tracking amplitude, frequency and load changes
- Very low power implementations


INTERFACE CIRCUIT DESIGN

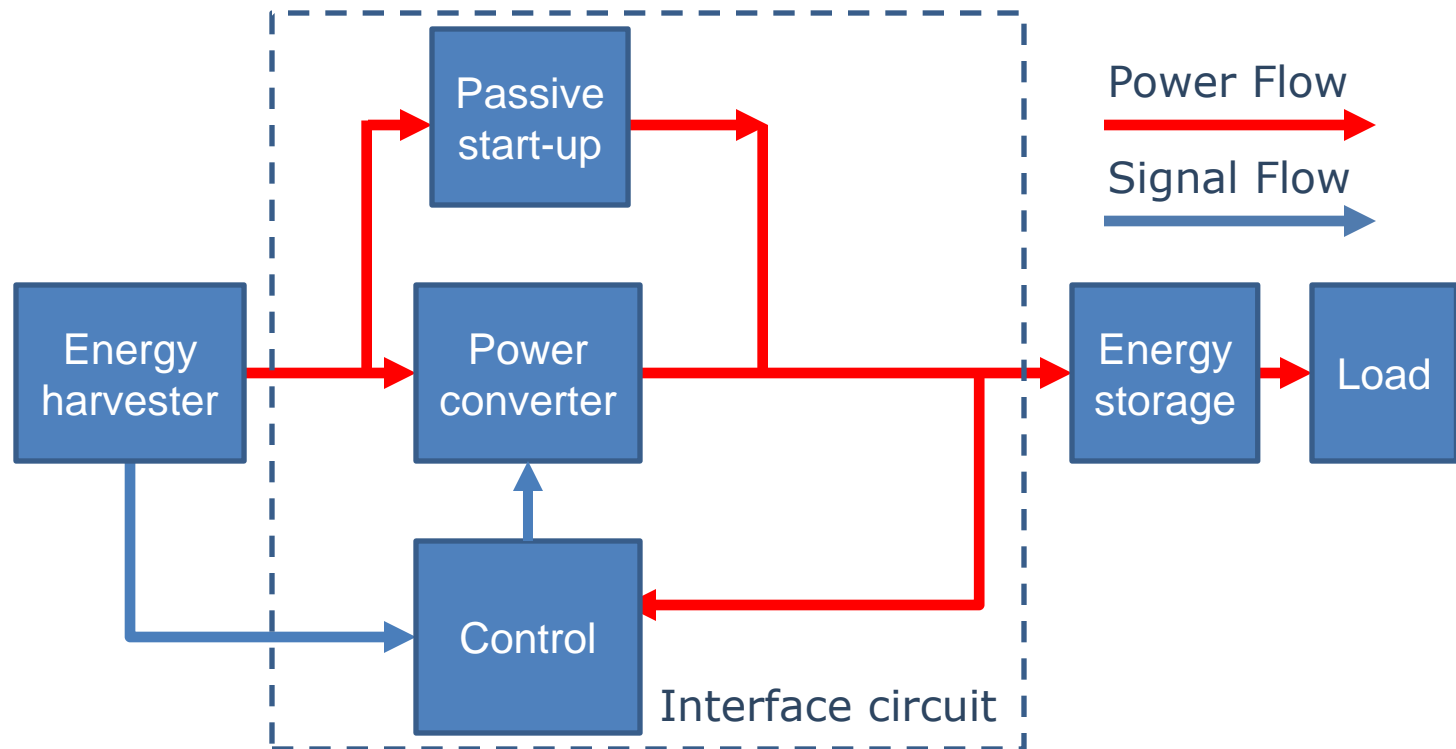- Rectification and Voltage Boosting
 - The harvester generates low-amplitude ($<1V$) AC voltage
 - The load requires $2V - 4.5V$ DC voltage
- Zero energy start-up



MATCHING CIRCUIT INPUT IMPEDANCE TO HARVESTER

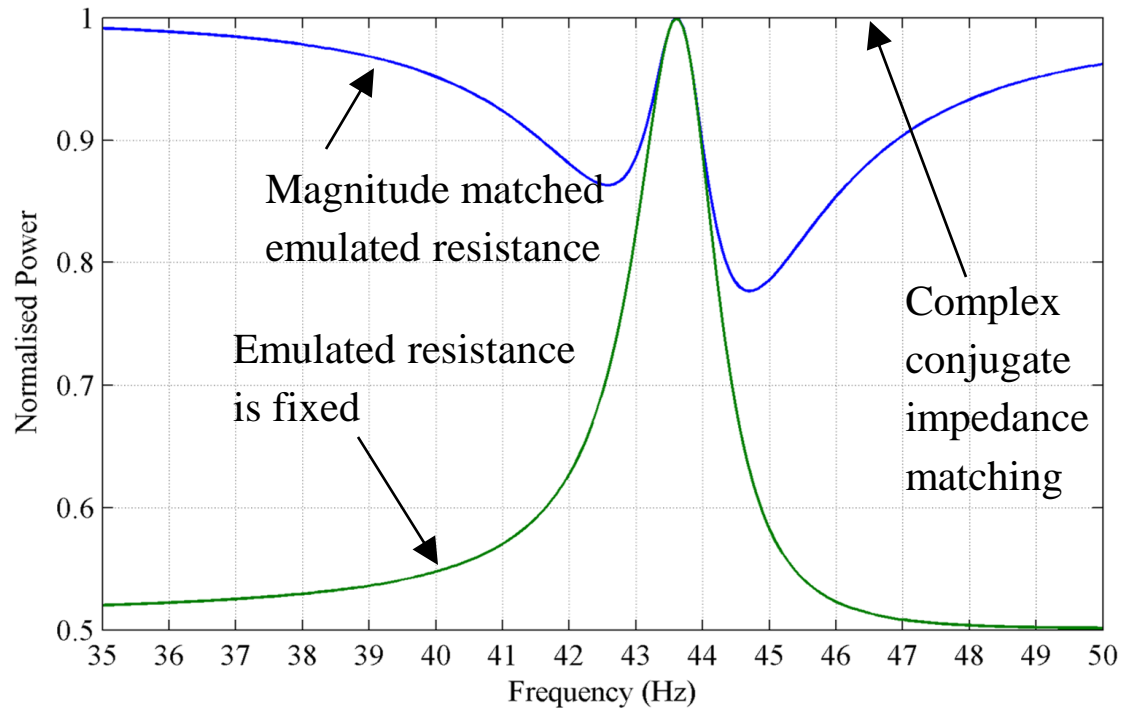
- Maximum power is extracted at matched impedances
- Harvester impedance is a function of the frequency
- Complex conjugate impedance matching requires high quiescent power for implementation
- Power close to the theoretical maximum can be extracted when the emulated resistance matches the magnitude of the source impedance



Power extracted with fixed load (green) and load adaptive to the frequency (blue)

CONVERTER CONTROL

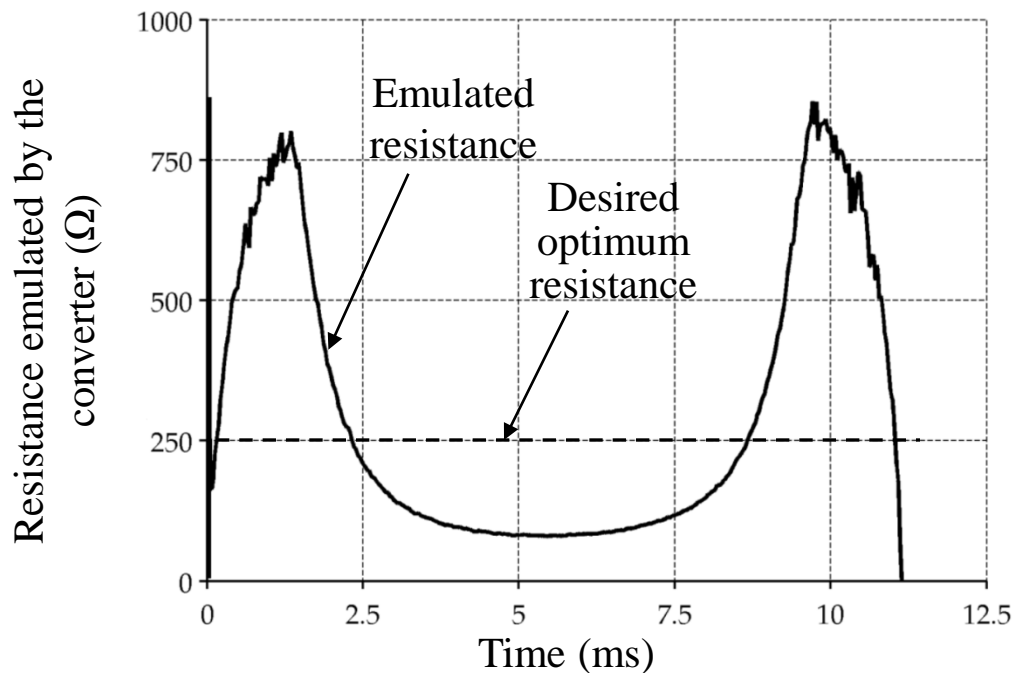
- The input impedance of the converter is a function of the instantaneous input and output voltages
- For maximum power extraction the impedance should be fixed during the harvester cycle and equal to the optimum




Emulated resistance during one harvester half-cycle at a constant duty ratio of the converter, the variation is caused by variation in the input voltage

MAXIMUM POWER TRANSFER TRACKING

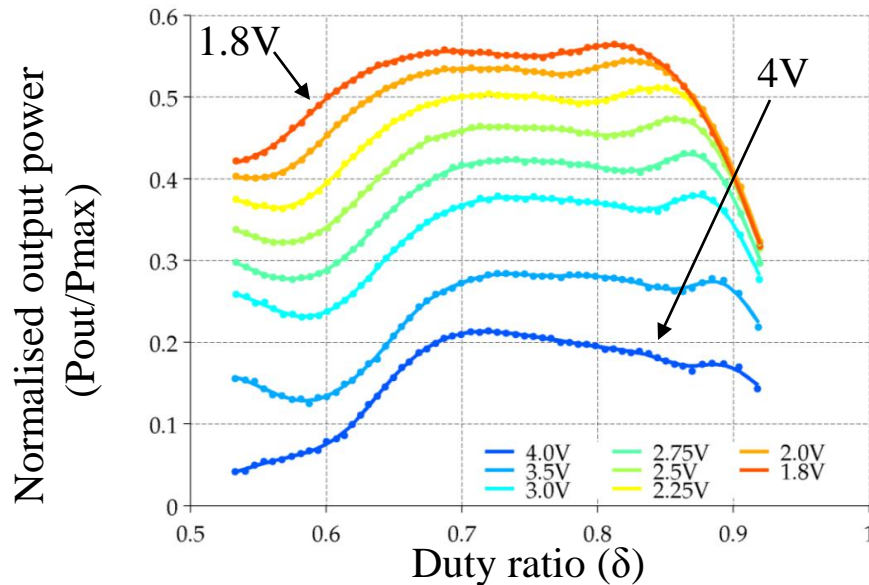- The power delivered to the load is a function of the extracted power and the conversion efficiency
- The optimum operating point is a function of the excitation magnitude and the output voltage



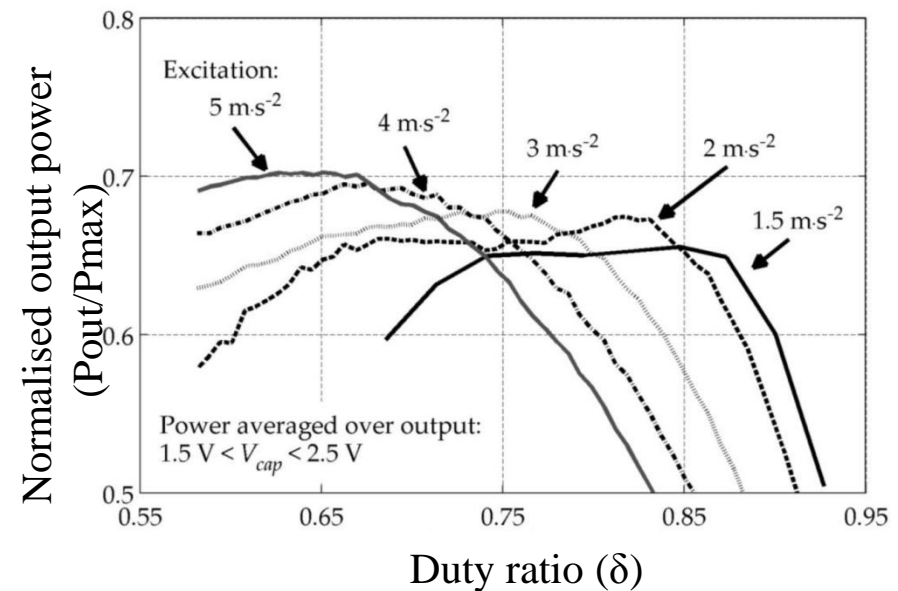
Output power as a function of the duty ratio at different output voltages, acceleration is constant (200 mg)



Output power as a function of the acceleration averaged over output voltage levels from 1.5 to 2.5 V

LOW POWER IMPLEMENTATION

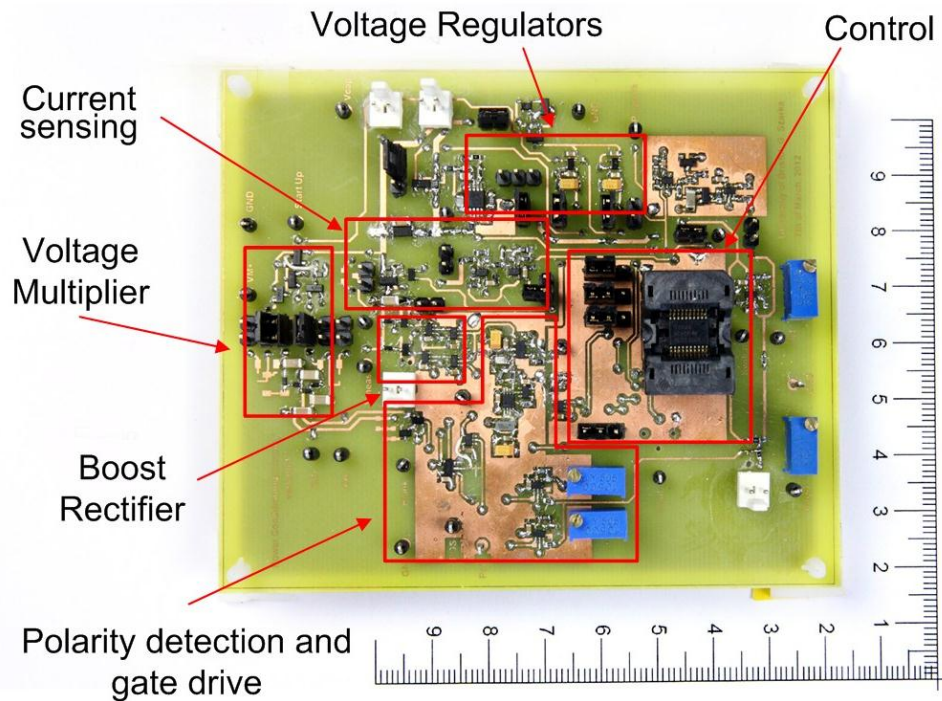- All functional requirements should be implemented at very low power which will allow for miniaturization of the harvester
- To achieve low-power operation:
 - The quiescent consumption should be as low as possible
 - The conversion efficiency should be maximised




Implementation of high-efficiency ultra-low-power adaptive interface circuitry for energy harvesting

Power electronics

Adaptive operation example:

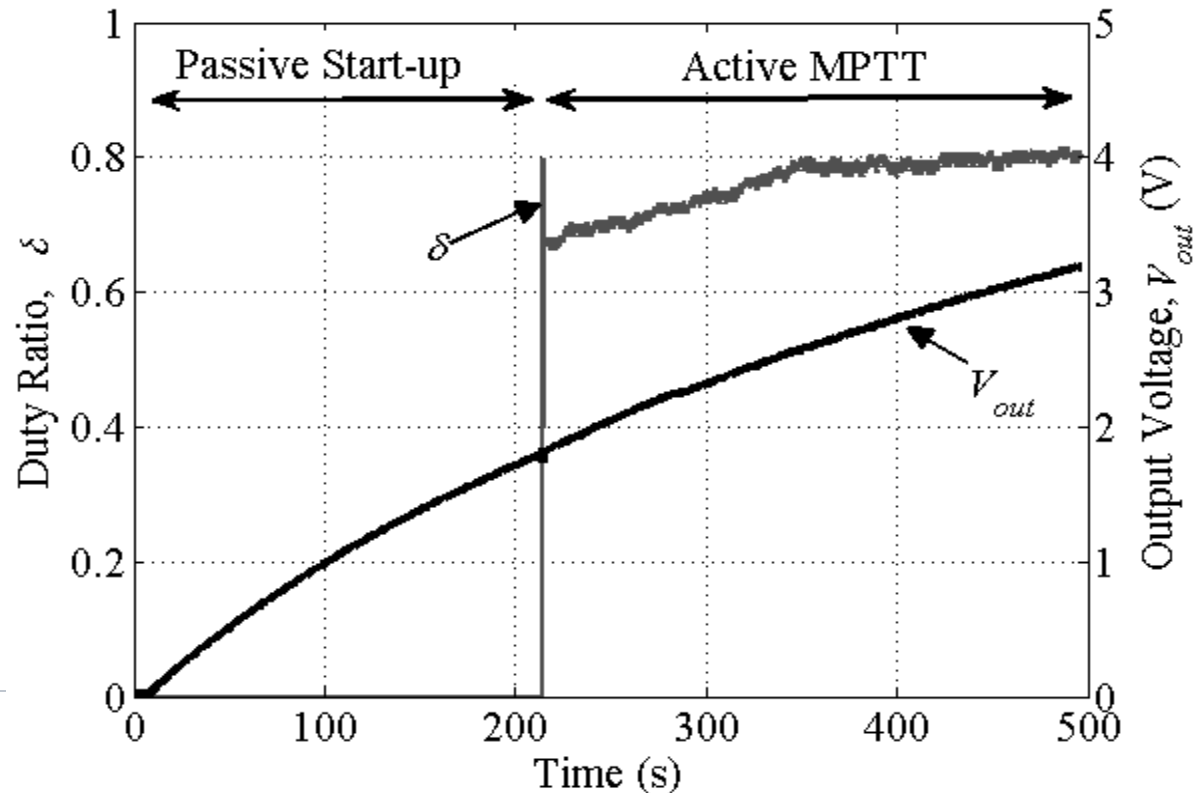
- Acceleration of the input excitation: $3.75 \text{ m}\cdot\text{s}^{-2}$
- Charging 68 mF capacitor from 0 V to 3.3 V
- The digital control becomes operational at 1.8 V and MPTT finds the optimum duty-ratio



Power electronics


Adaptive operation example:

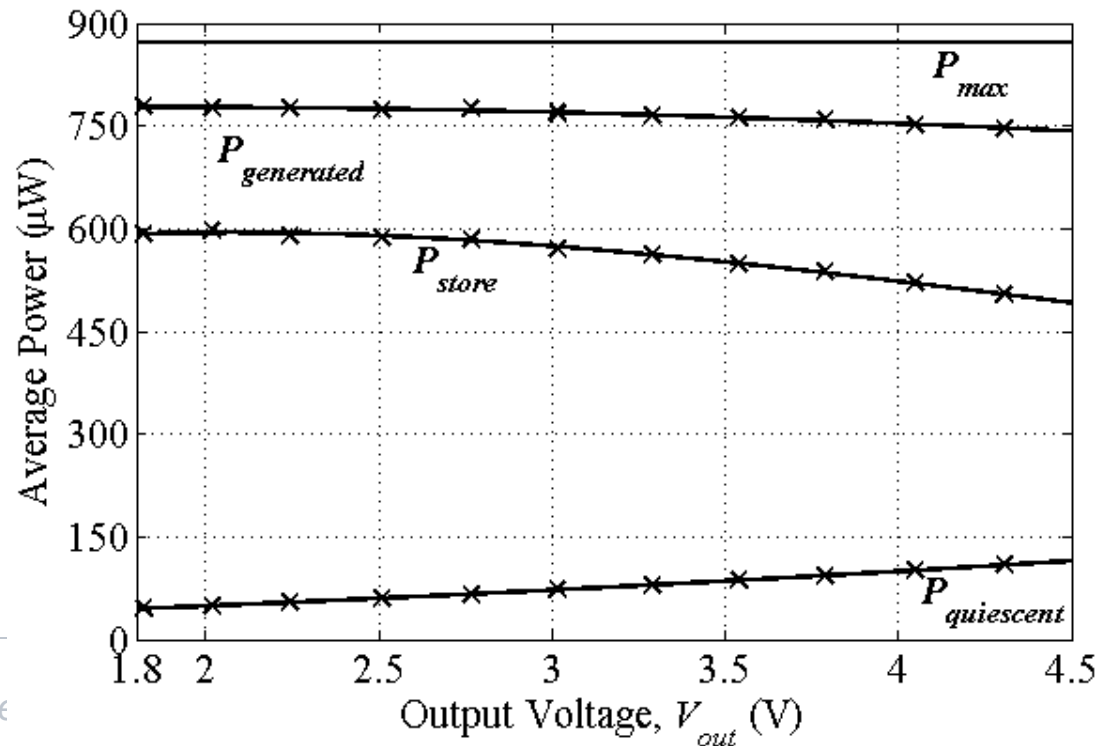- Output power is a function of the input power and the efficiency of the converter
- MPTT maximises the output power
- Average overall efficiency (ratio between the output power P_{store} and theoretical maximum power P_{max}) – 0.7-0.75%




Improving the adaptiveness of the system

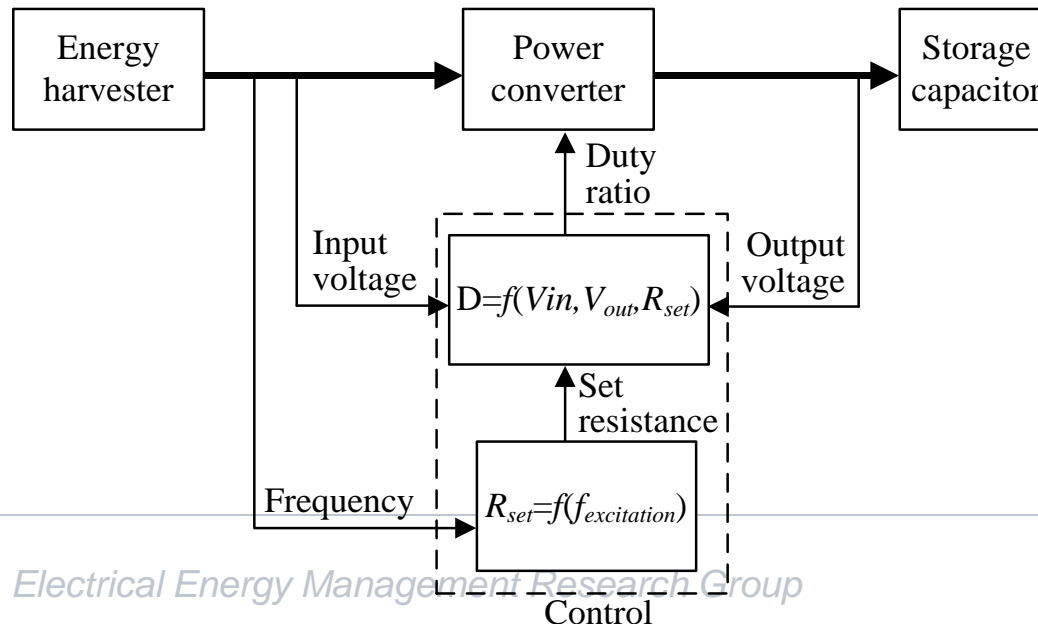- Instantaneous optimisation corresponding to variations of the input and output voltages – ensures the input resistance of the converter is not affected by variations of the input and output voltages
- Response to changes in the frequency of the excitation – the new optimum point can be determined by measuring the frequency



Constant resistance emulation

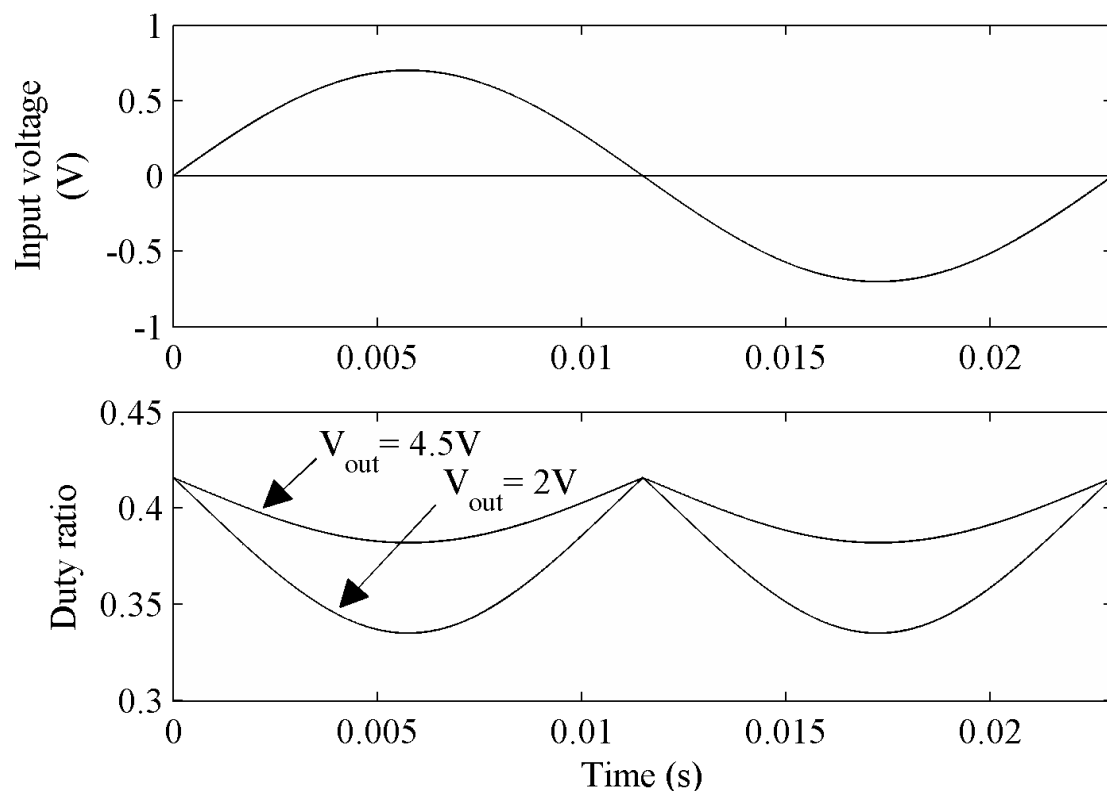- Duty ratio required to maintain constant resistance during one cycle :




- $V_{in\ pk} = 0.6\ V$
- $V_{out} = 2\ V, 4.5\ V$

- Maximum variation of the required duty ratio: 17%


Fixed resistance emulation

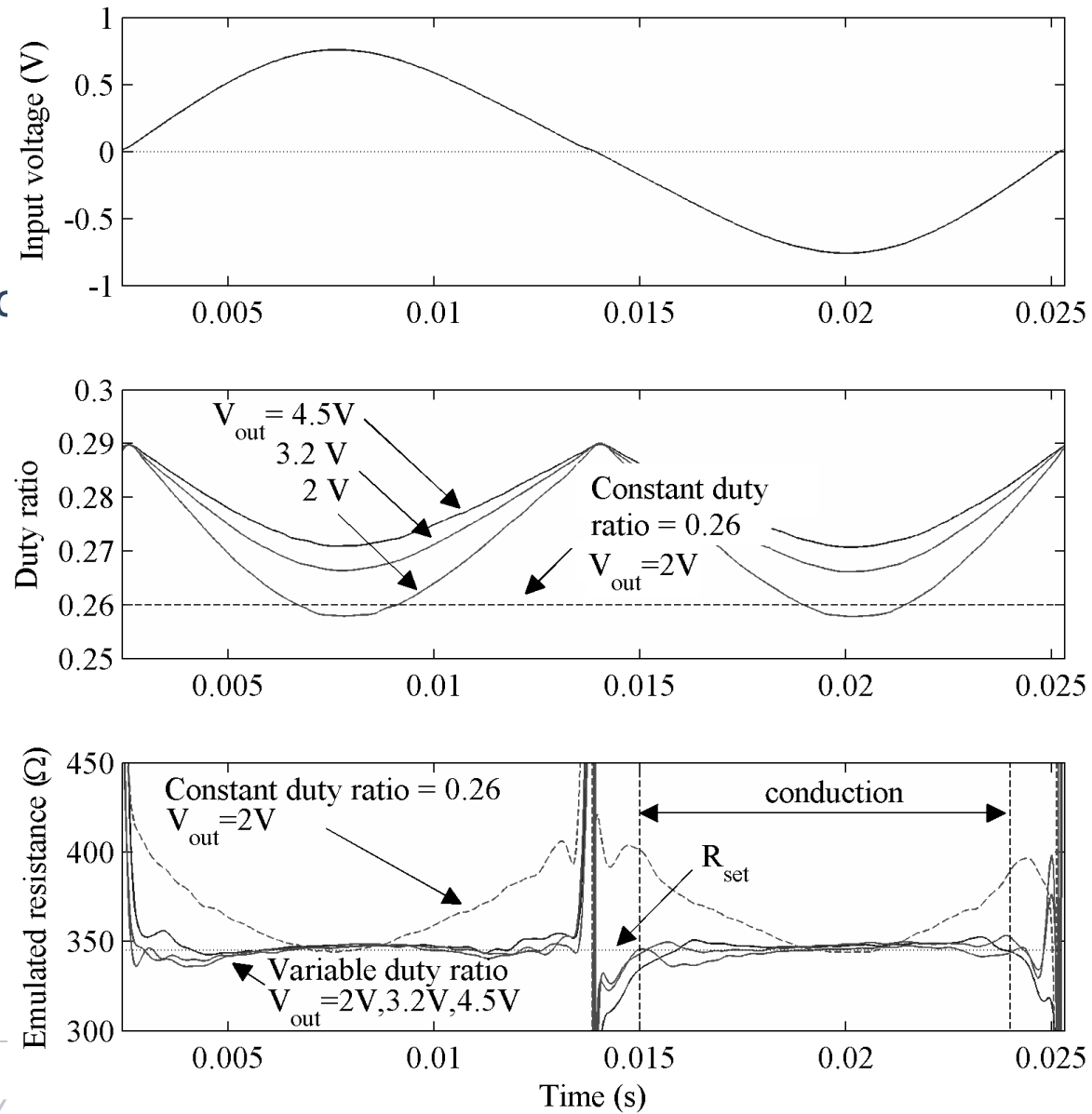- Emulated resistances for different output voltages with variable duty ratio compared to constant duty ratio
- Constant duty ratio results in 15% maximum deviation from the optimum resistance during the period of conduction



Magnitude matching

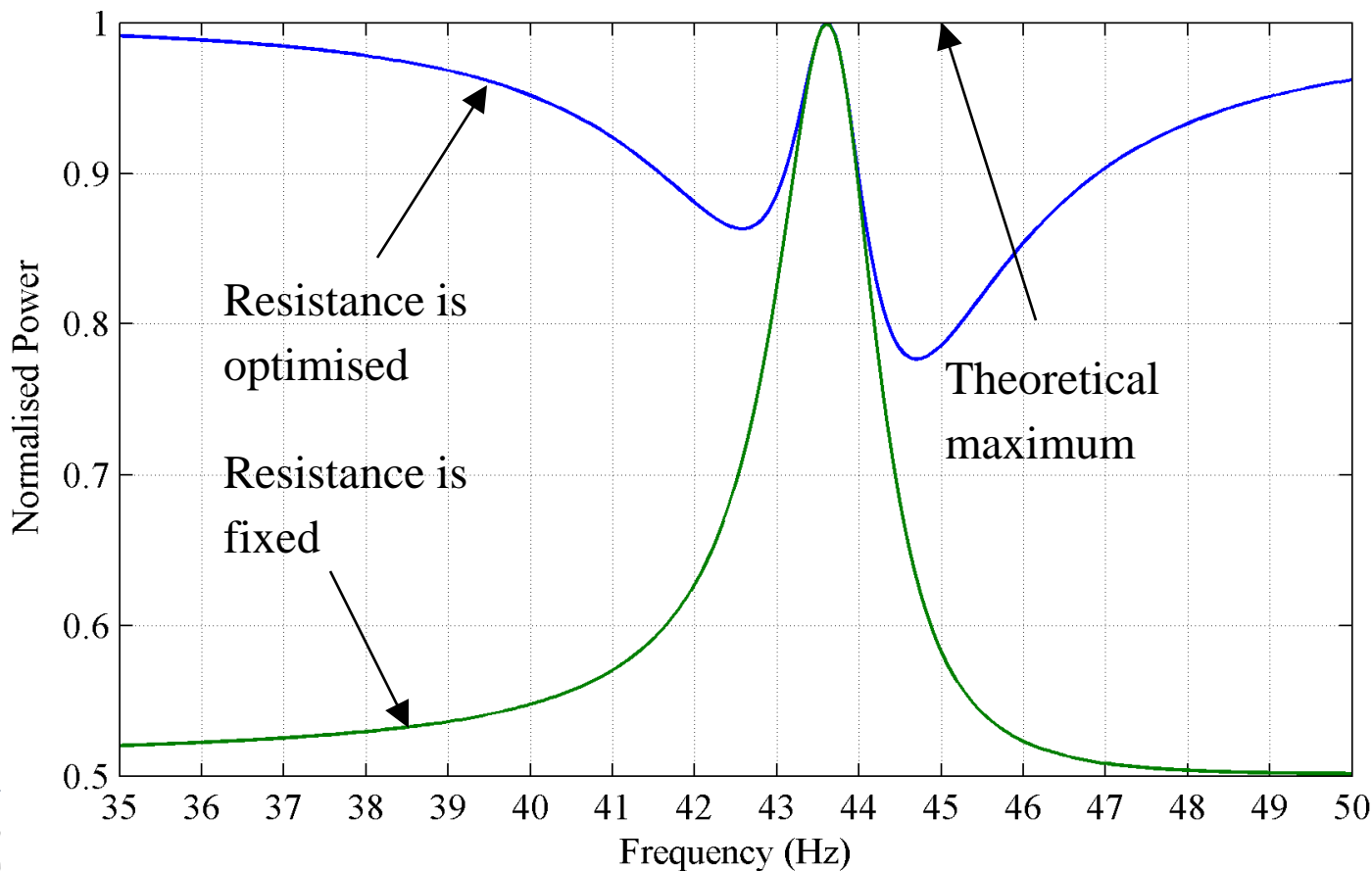- Optimising the input resistance of the converter to match the magnitude of the source impedance.



Emulated Resistance

- Measured resistance (x) compared to the theoretical optimal resistance (-) for maximum power extraction with magnitude matching.

